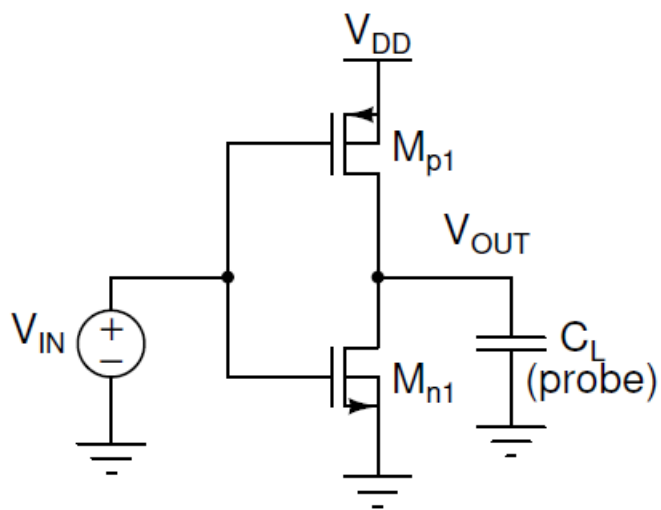


Experiment-8 Operational Amplifiers

Part 1:


(A) To plot the voltage transfer characteristics (V_{OUT} vs V_{IN}) and identify the valid input output region for the circuit to act as an amplifier.

Schematic circuit:




Where V_{DD} is 5 V.

Circuit:

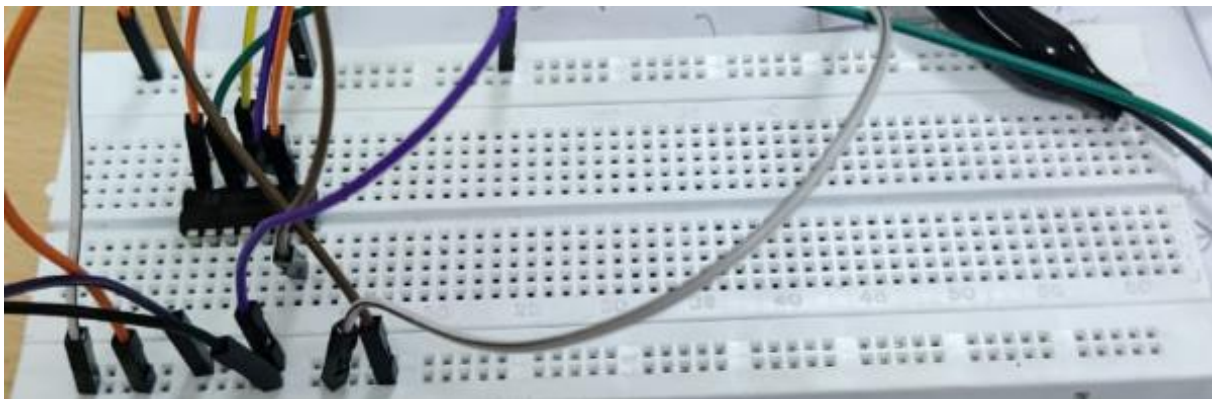

Plot:

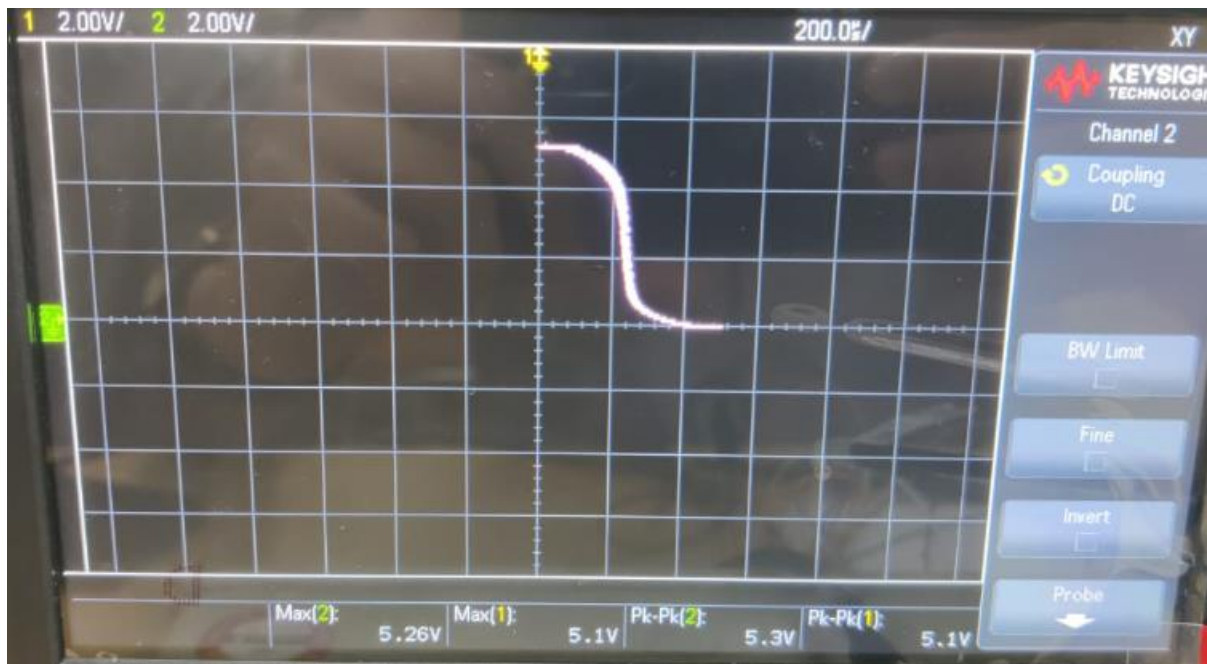


Approximate points where gain (Slope of graph) is greater than 1 in magnitude.



Start: $V_{IN} = 1.28125V$


End: $V_{IN} = 2.51250V$

(B) Schematic circuit:

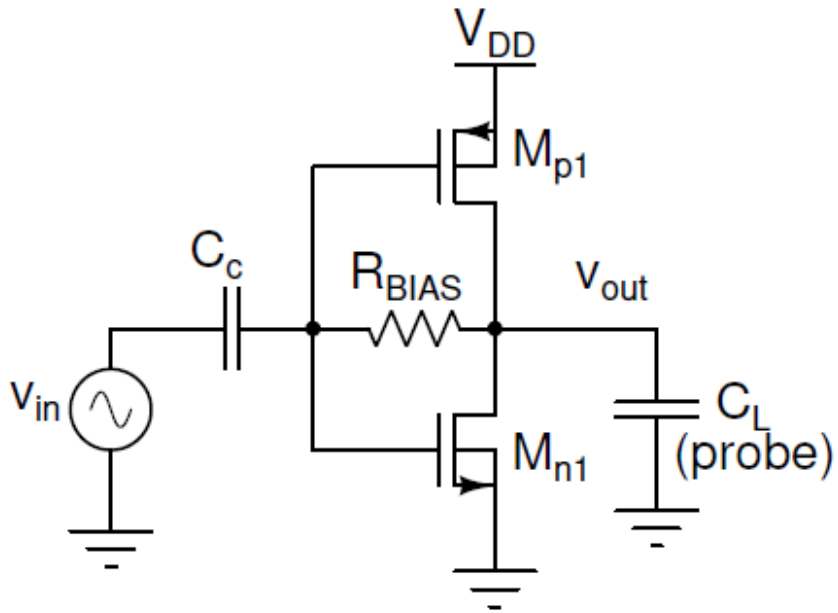


Observing gain of the circuit for different input values of V_{in} .


For V_{in} : 100mVPP

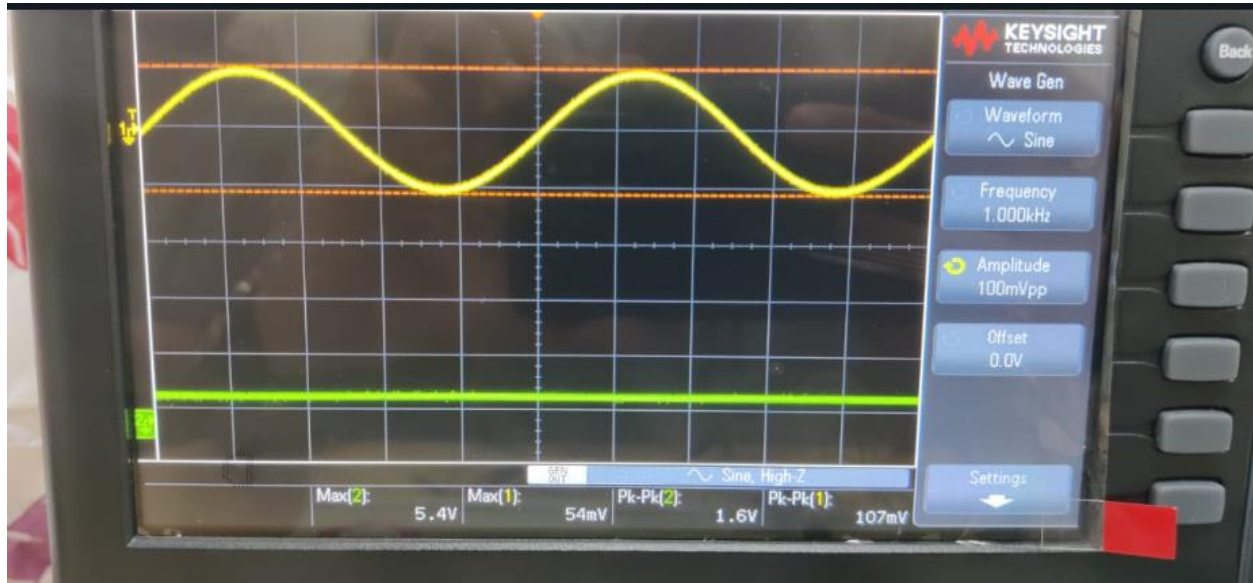


V_{in} : 200mVPP

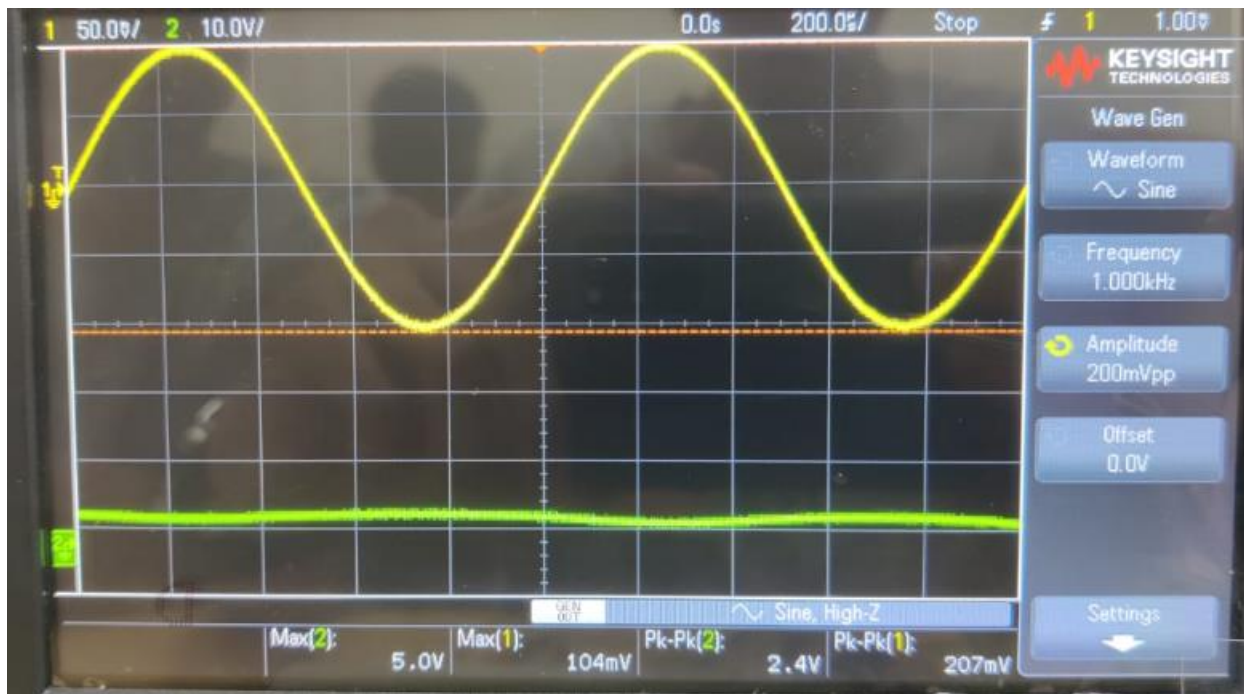


Vin: 300mVPP

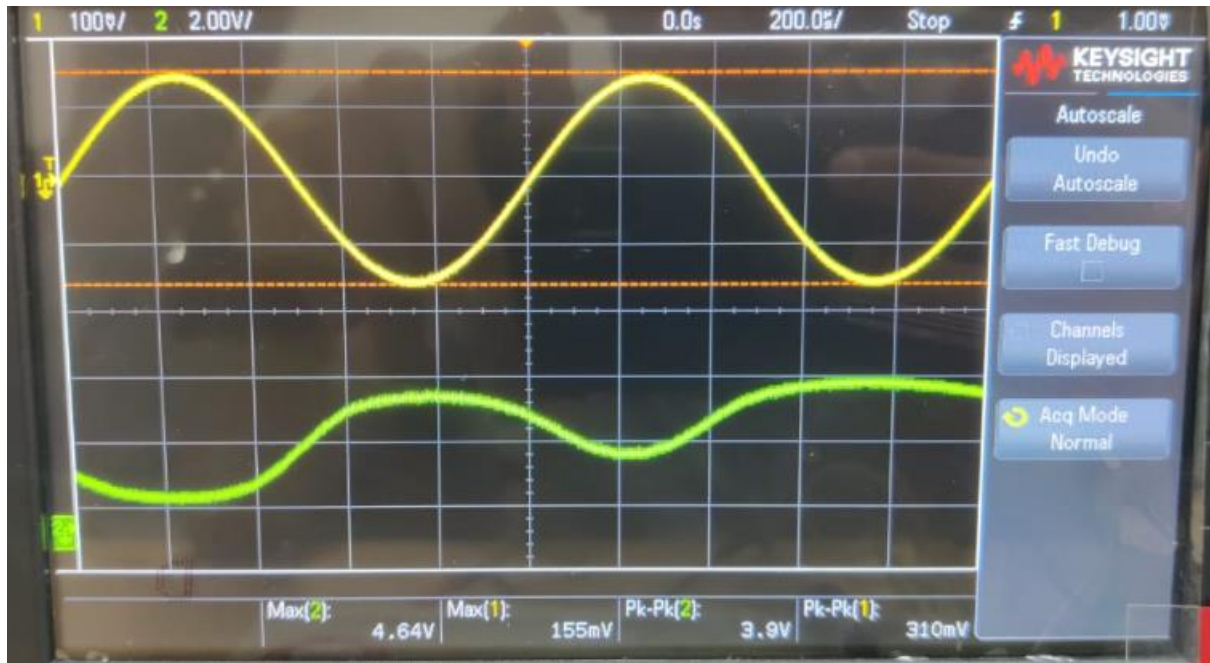

Vin: 400mVPP

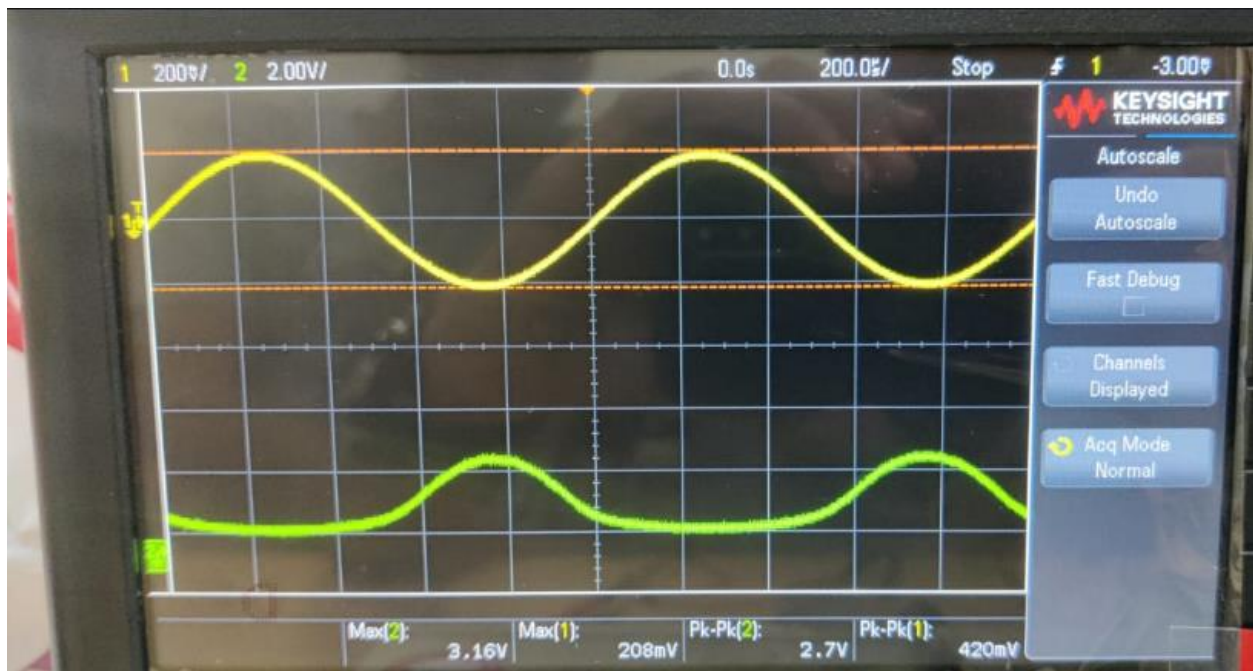

Vin :500mVPP

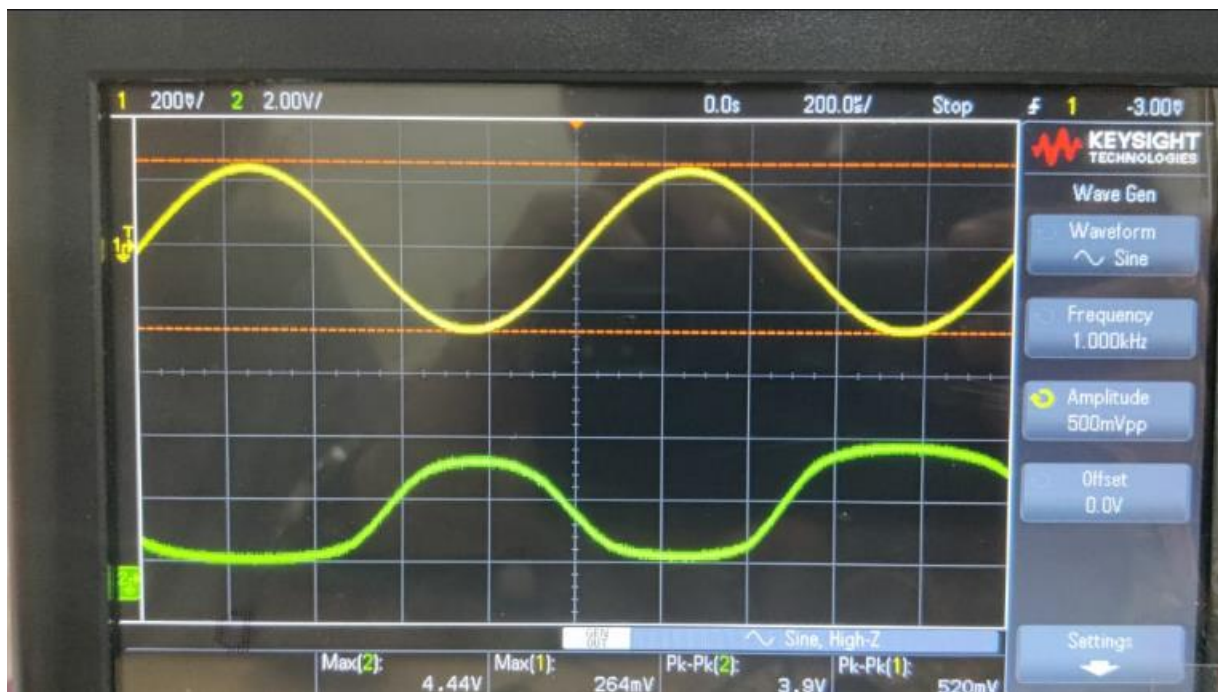

Vin (mVolts)	Vout (Volts)	Gain
--------------	--------------	------


100	1.6	16
200	2.4	12
300	3.9	13
400	2.7	6.75
500	3.9	7.8

There is a clip off because for higher values of V_{in} the circuit reaches in a region where $V_{in} - V_{th} > V_{out}$, hence it enters triode region hence we instead getting a sinusoidal input get a clip off.


DC values at gate= 756mV and drain= 100mV

2. Characterization of an operational amplifier


Schematic view of circuit:

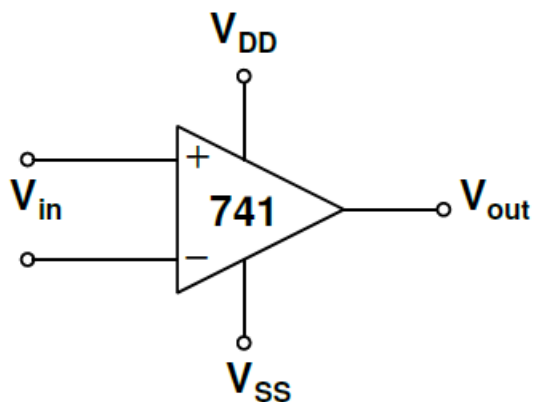


Opamp:

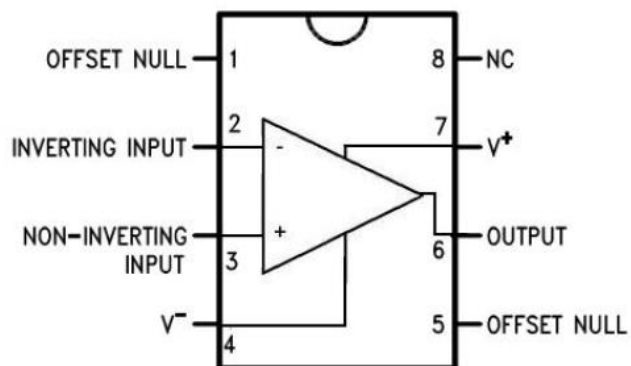

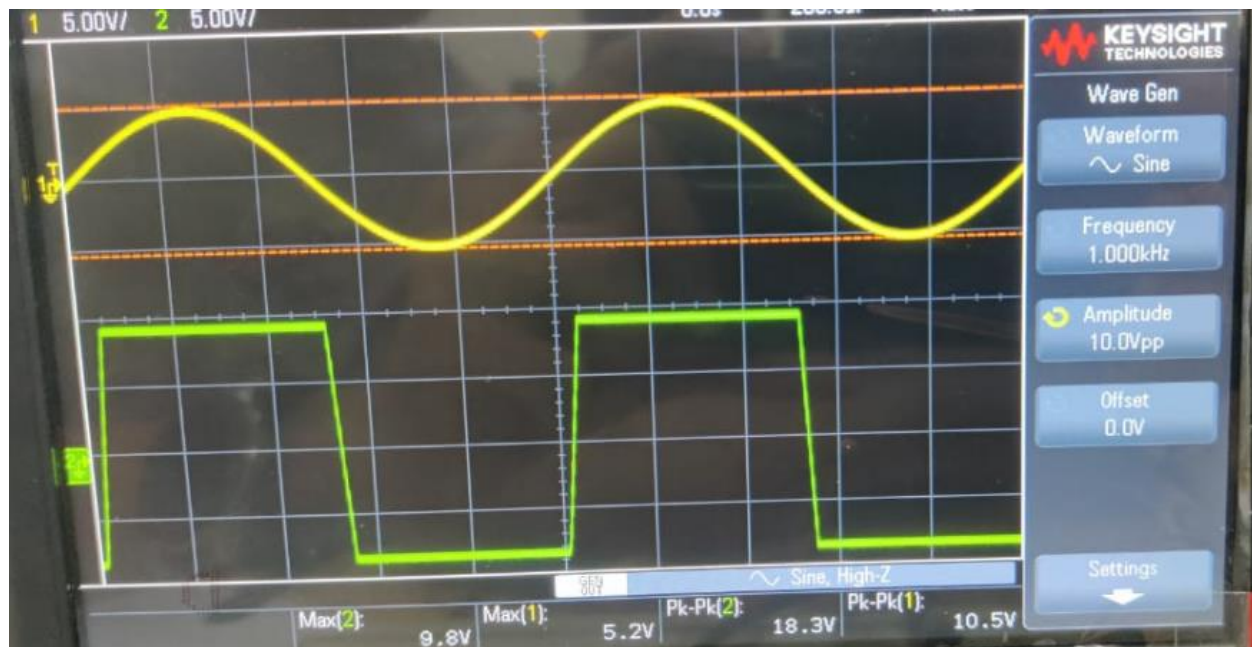
V_{in} : 10Vpp and frequency = 5 kHz and V_{DD} = 10 V, V_{SS} = -10 V




X-Y characteristic:

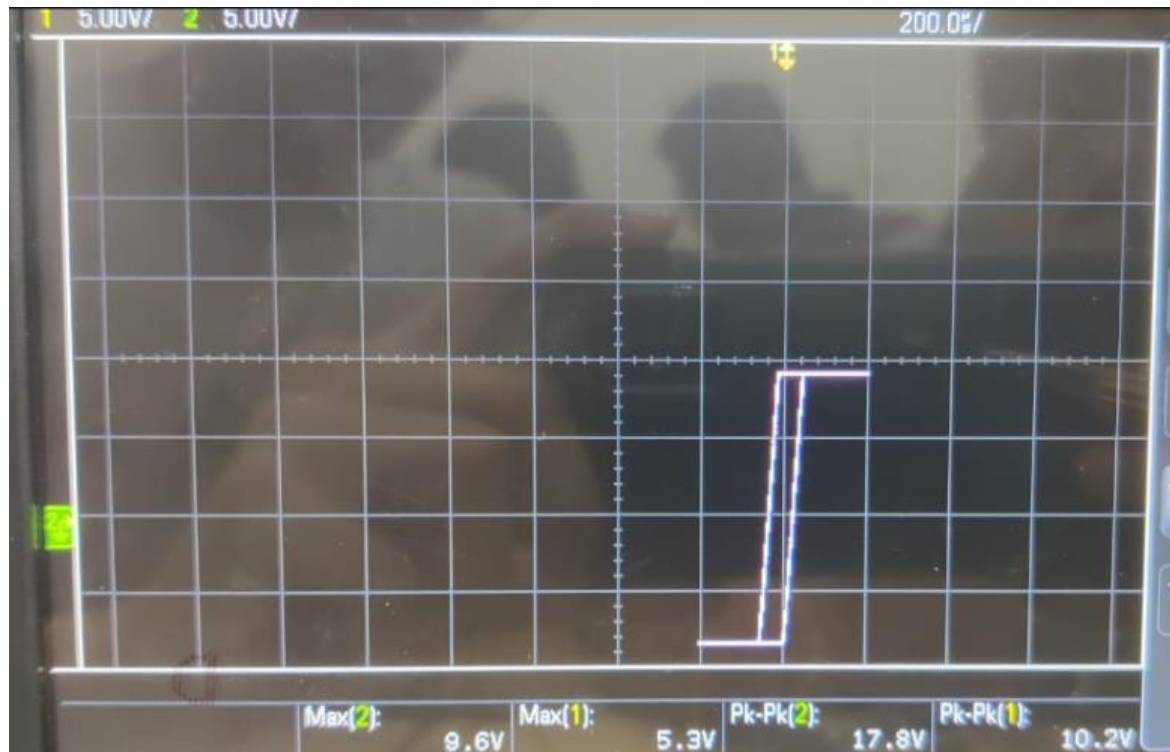


(B)

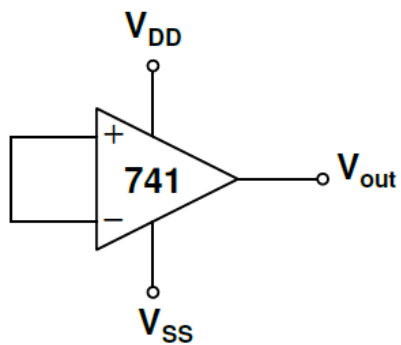

Output:

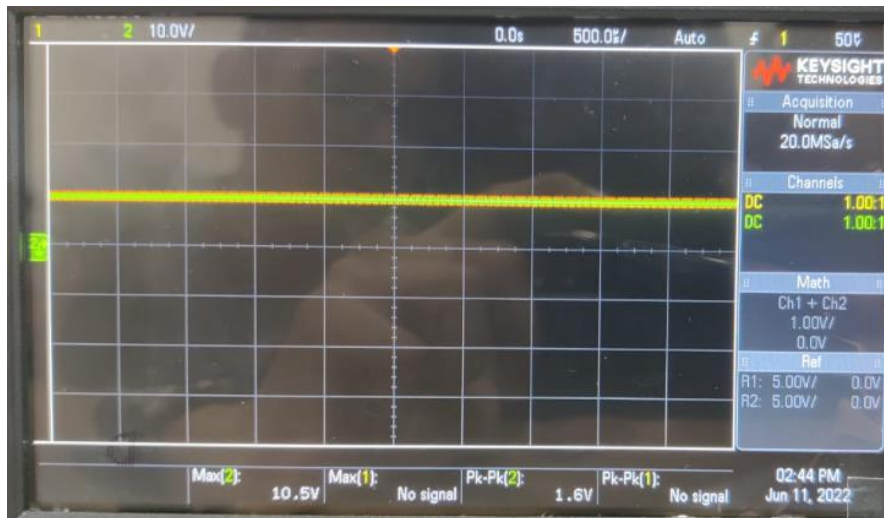

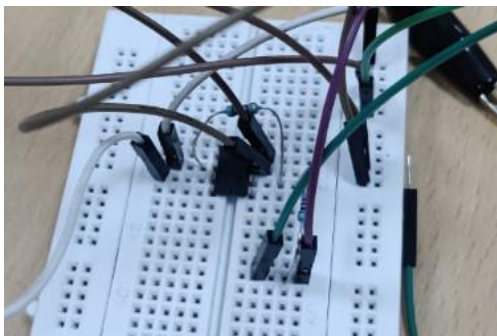
On reducing the DC voltage V_{DD} and V_{SS} to near 0.8V the DC off set in the output reduces to 0.



Circuit:

3. Non-inverting amplifier

schematic view of the circuit:

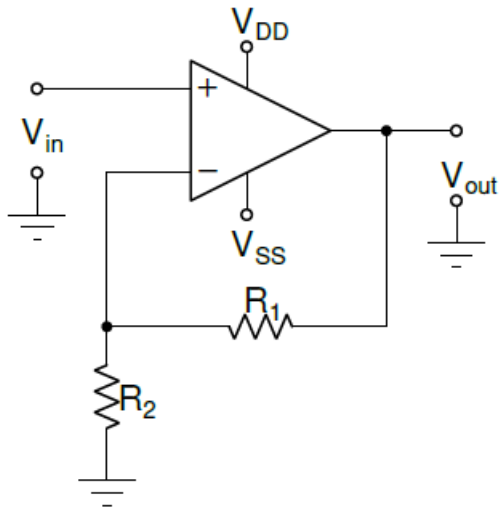

(A)

$$V_{in} = R_2 / (R_2 + R_1) * V_{out}$$

$$V_{out}/V_{in} = 1 + R_1/R_2.$$

Circuit:

(b) $V_{in} = 250\text{mV}$ and frequency = 5 kHz from the function generator, $V_{DD} = 12\text{ V}$, $V_{SS} = -12\text{ V}$


R1	R2	Vout	Gain(theoretical)	Gain(Practicall)
10K	10K	530mV	2	2.12
10K	4.7K	840mV	3.127	3.218

Gain of amplifier when R1 and R2 are shorted is 1.


The voltage follower or unity gain buffer is a special and very useful type of **Non-inverting amplifier** circuit. The use of voltage follower is that it has got very **high input impedance** and very **low output impedance**, which makes it a perfect circuit for **impedance matching**.

Plots:

$R_1 = R_2 = 10K$

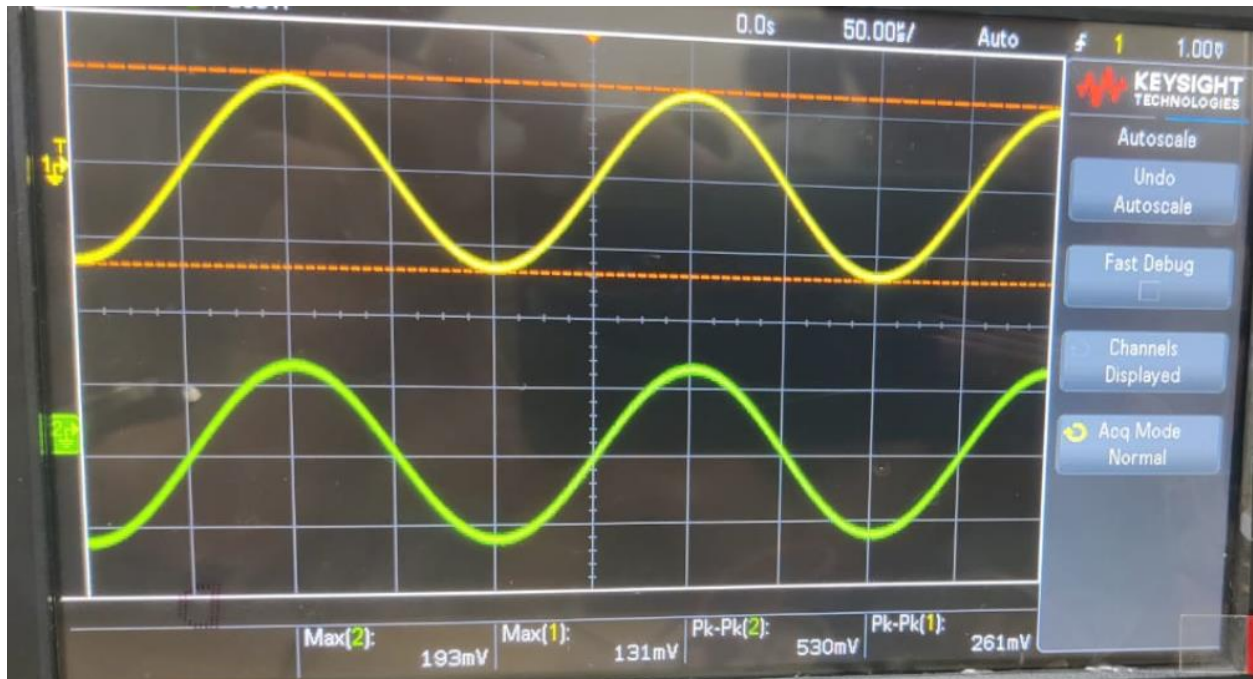


$R_1 = 10K, R_2 = 4.7K$

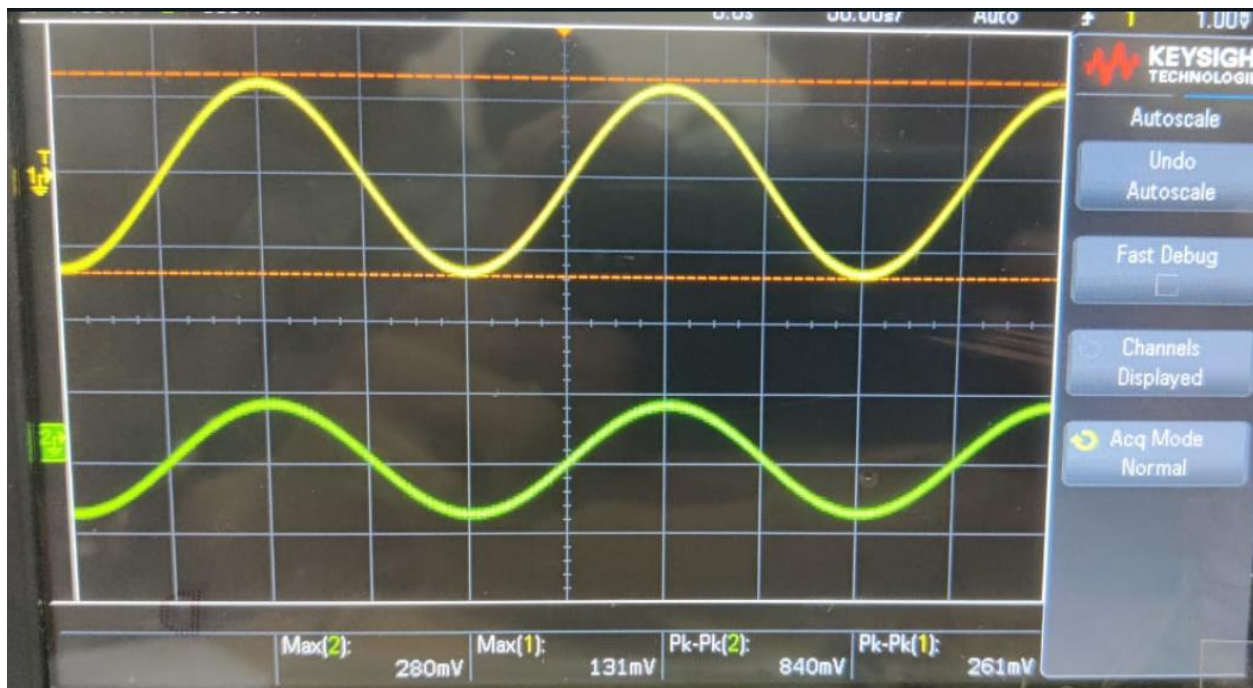


Expected gain	R1	R2	Vout	Gain
4	30K	10K	1.01 V	4.04
5	39K	10K	1.27 V	5.08

R1 = 30K, R2 = 10K

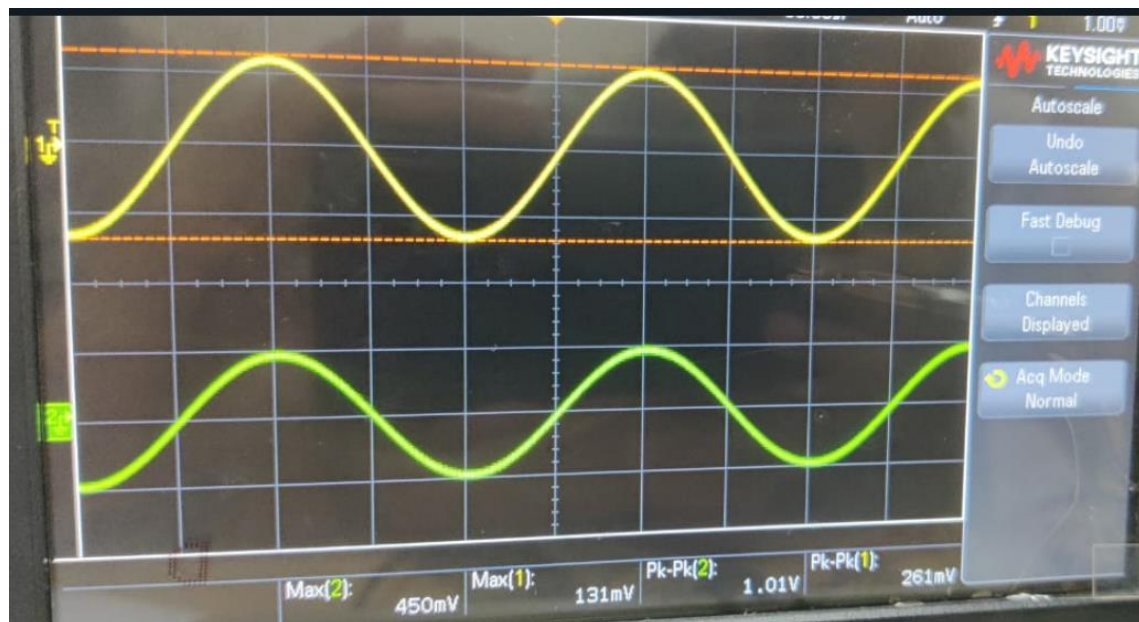


R1 = 39K, R2 = 10K

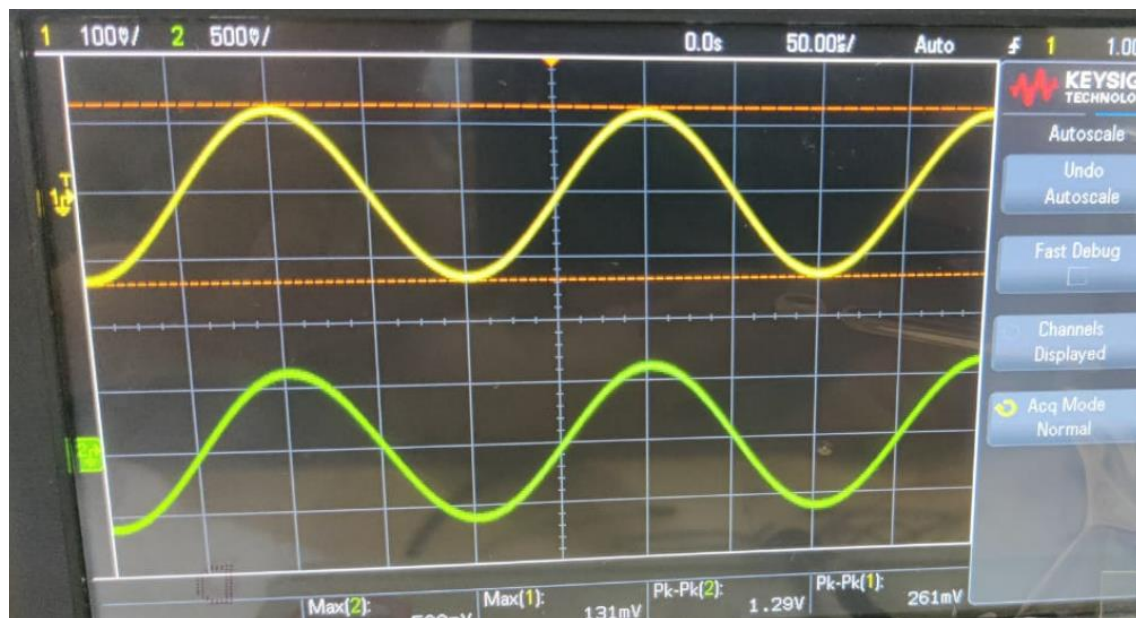

4. Inverter amplifier

schematic view of the circuit:

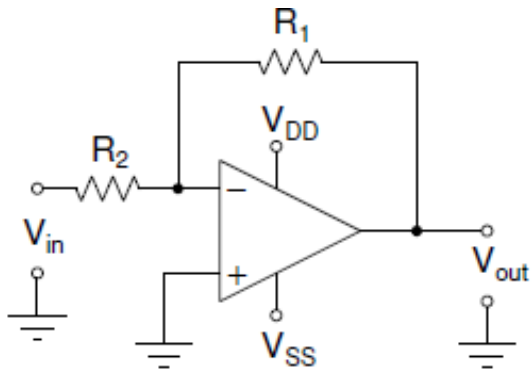

Deriving gain relation:

Let current through R2 be i

$$I = (V_{in} - V_{out}) / R_2 + R_1$$

Let v2 be voltage at common node of R1 and R2.

$$I = (V_{in} - V_2)/R_{in} = (V_2 - V_{out})/R_f$$

$$V_{in} / R_2 = V_2[1/R_2 + 1/R_1] - V_{out}/R_1$$


$$I = (V_{in} - 0)/R_2 = 0 - V_{out} / R_1$$

$$V_{out} / v_{in} = -R_1 / R_2.$$


R1	R2	Vout	Gain(Theoretical)	Gain(Practical)
10K	10K	261mV	1	1.044
10K	4.7K	550mV	2.12	2.2

Gain	R1	R2	Vout	Gain(Practical)
4	40K	10K	1.03V	4.12
5	50K	10K	1.33V	5.32


Gain: 1

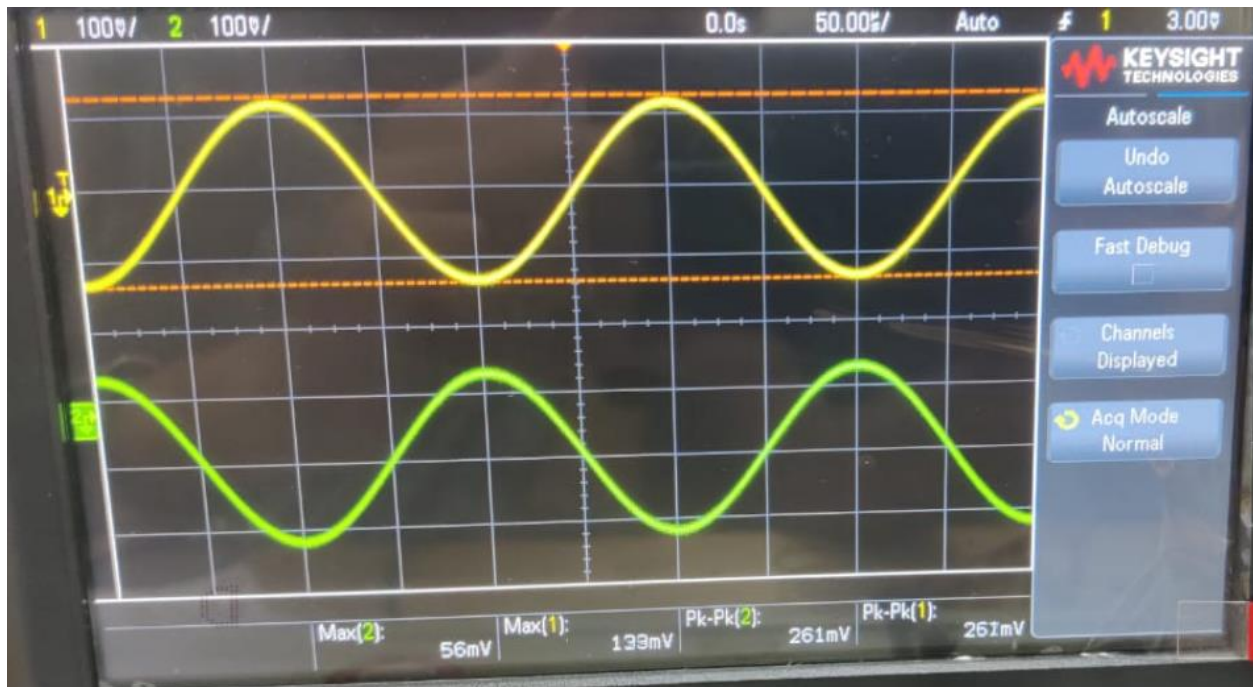

Gain: 2.12

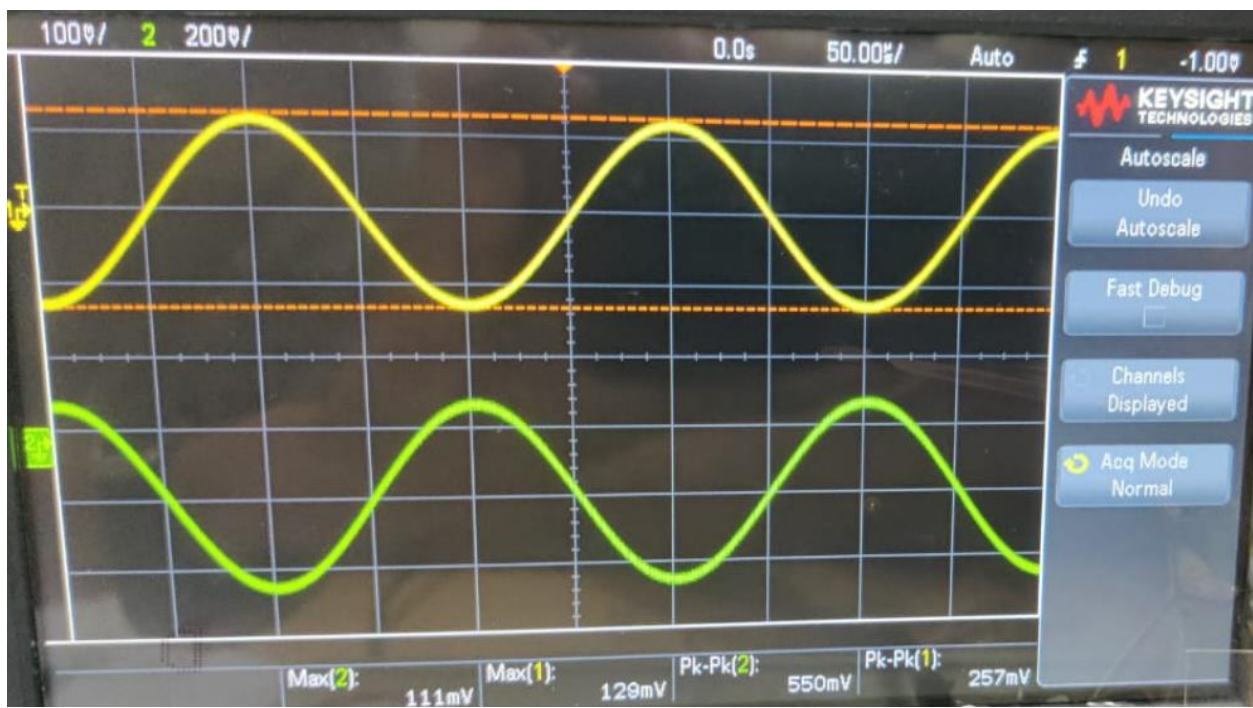

Gain: 4

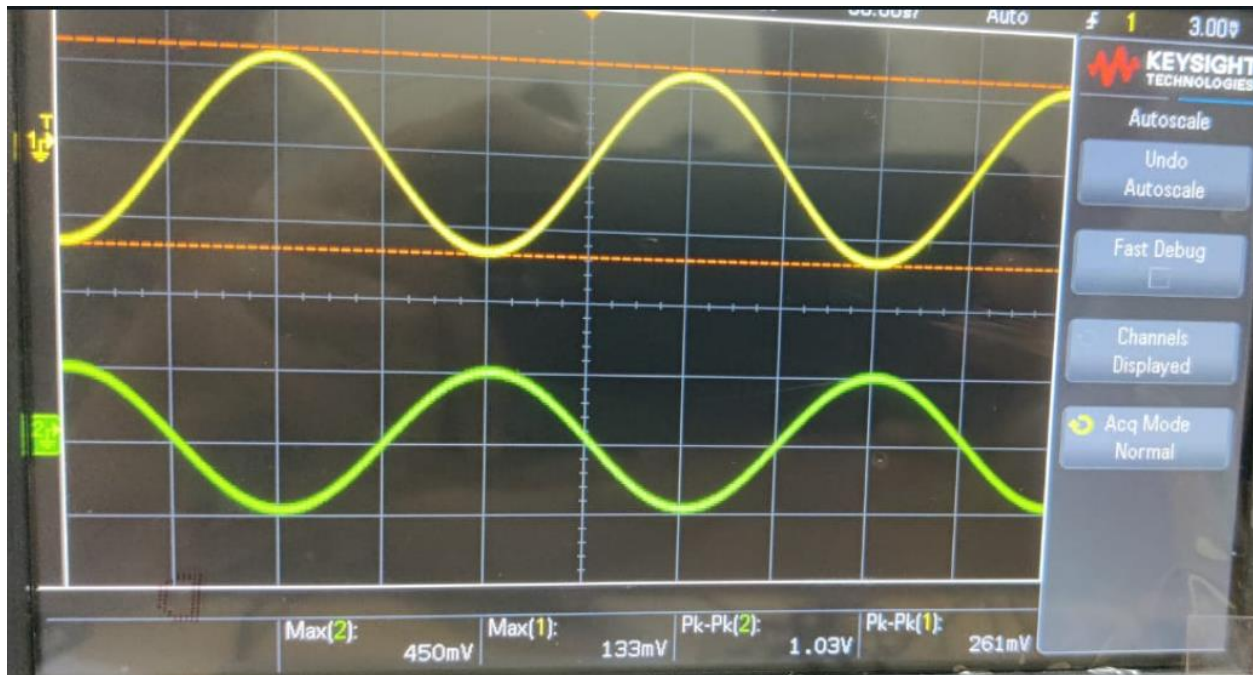

Gain: 5

