

Experiment-3

Full Wave Rectifiers

1. Transformer Characterization

Schematic circuit:


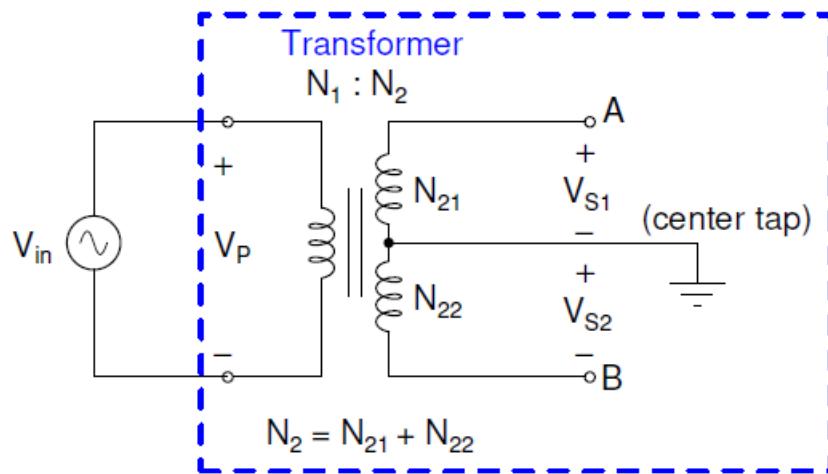


Figure 1: Bridge Rectifier

Circuit:

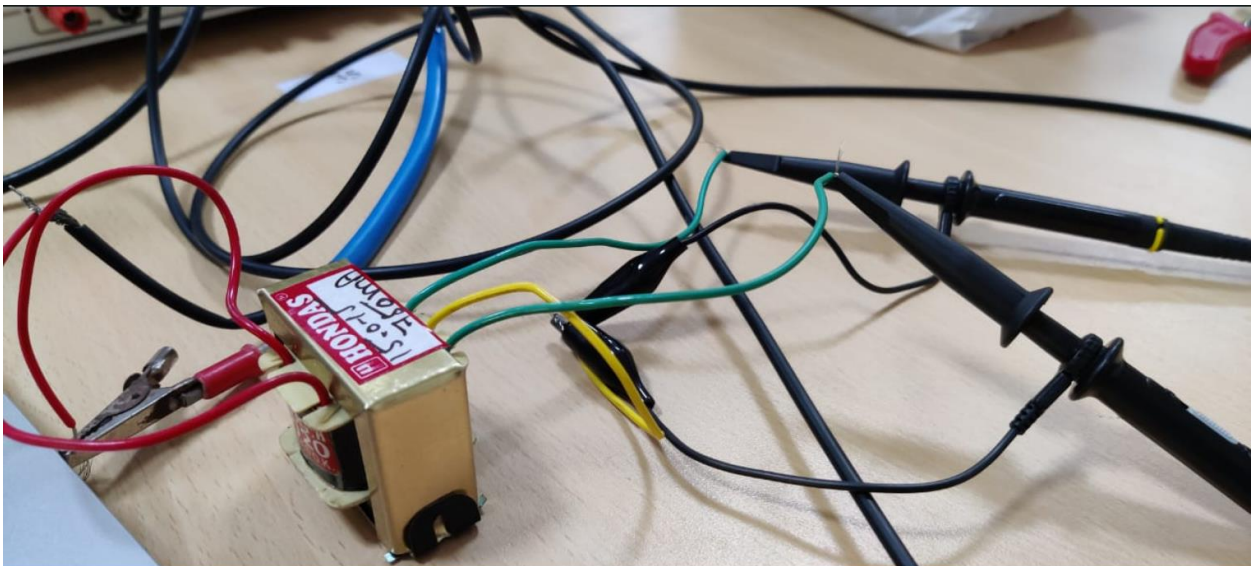

(b) Plotting and noting amplitude and phase difference between V_A and V_B :




$V_A \rightarrow$ Amplitude $\rightarrow 460\text{ mV}$, $\phi = \text{same as input wave}$.
 And
 $V_B \rightarrow$ Amplitude $\rightarrow 460\text{ mV}$, $\phi = -180^\circ + (\phi) \text{ input}$
 \therefore frequency = 1 kHz

b) Amplitude : $V_A = V_B$ ($\because N_1 = N_2$)
 ϕ (phase) $\Rightarrow \boxed{\phi_A - \phi_B = 180^\circ}$


c)

Input frequency	Amplitude (V _A)
1 KHz	460 mV
10 KHz	440 mV
50 KHz	470 mV
100 KHz	0.635 V
1 MHz	0.645 V
5 MHz	320 mV
10 MHz	220 mV
20 MHz	180 mV


1-> 10 KHz:

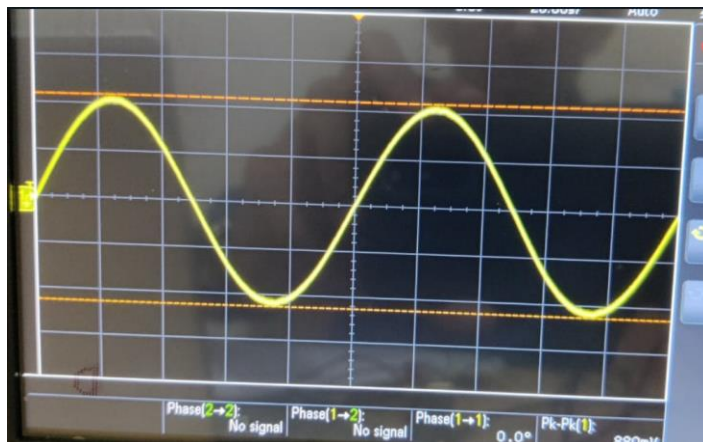


2->50 KHz:

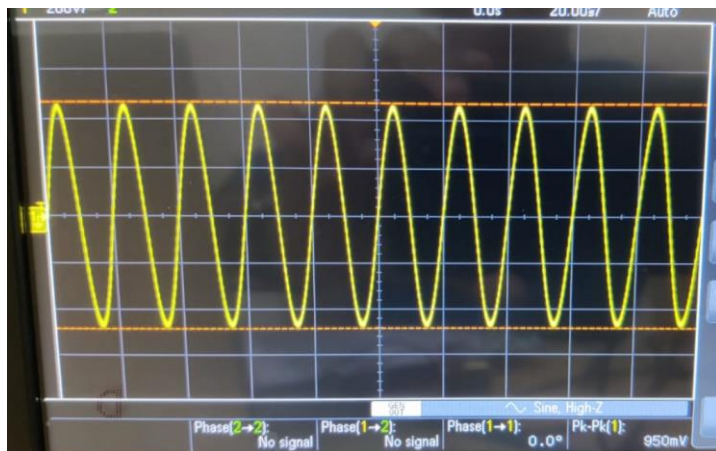

3->100kHz

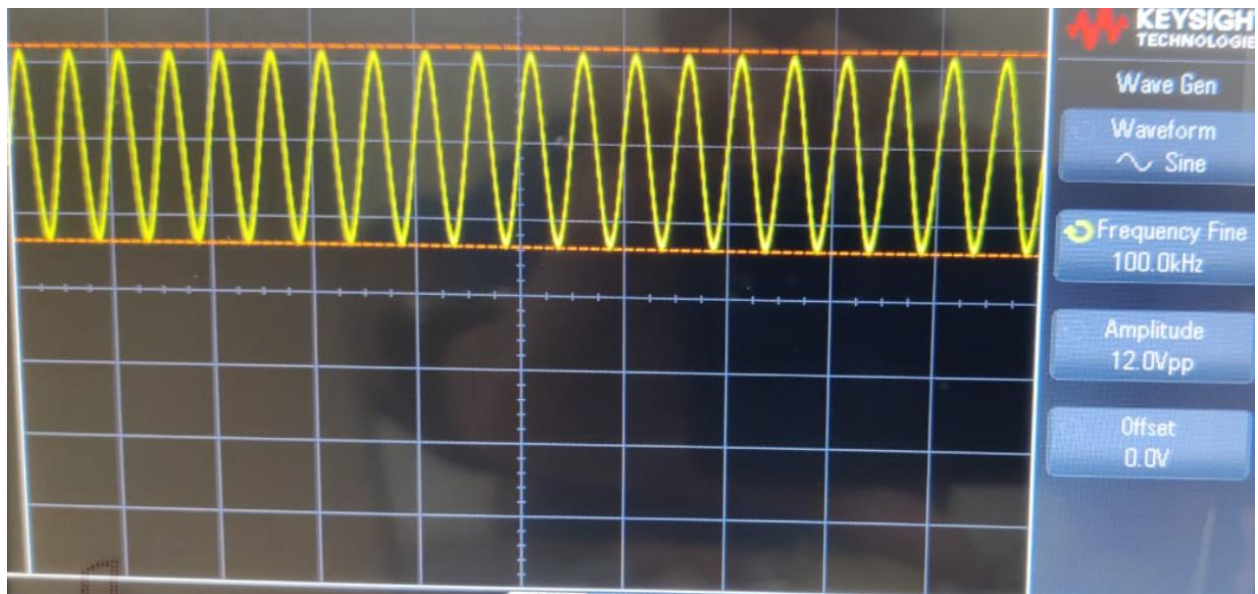


4->1Mhz

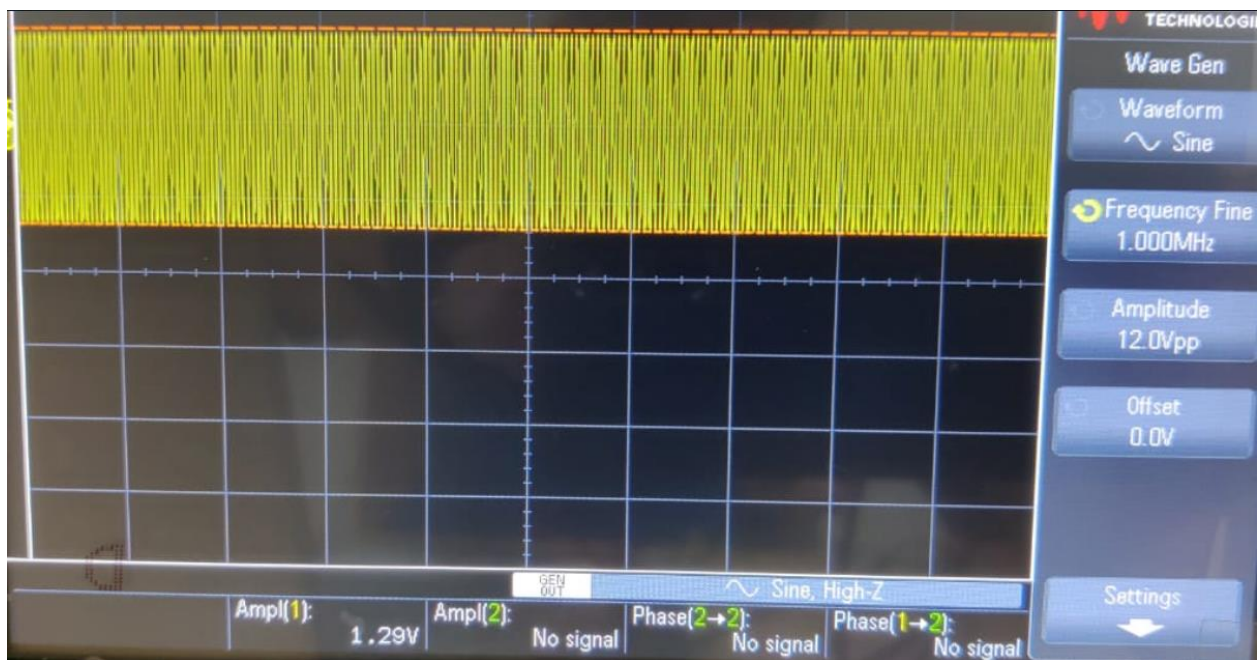


5->5MHz



6->10Khz

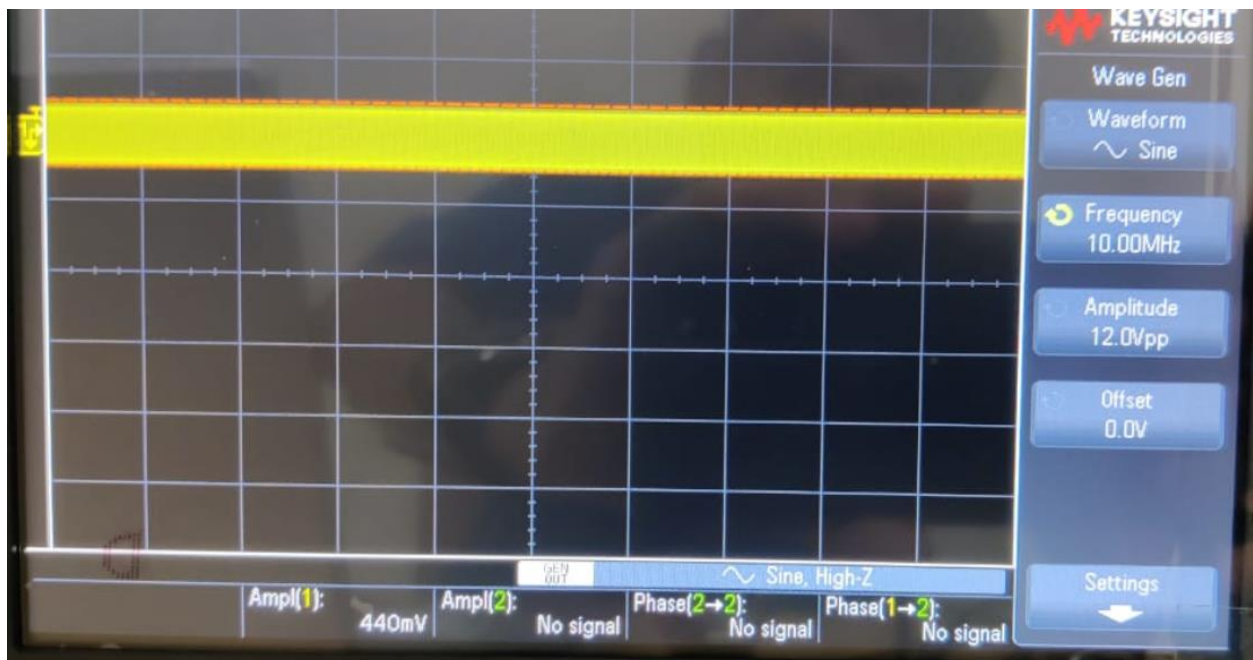

7->20Mhz

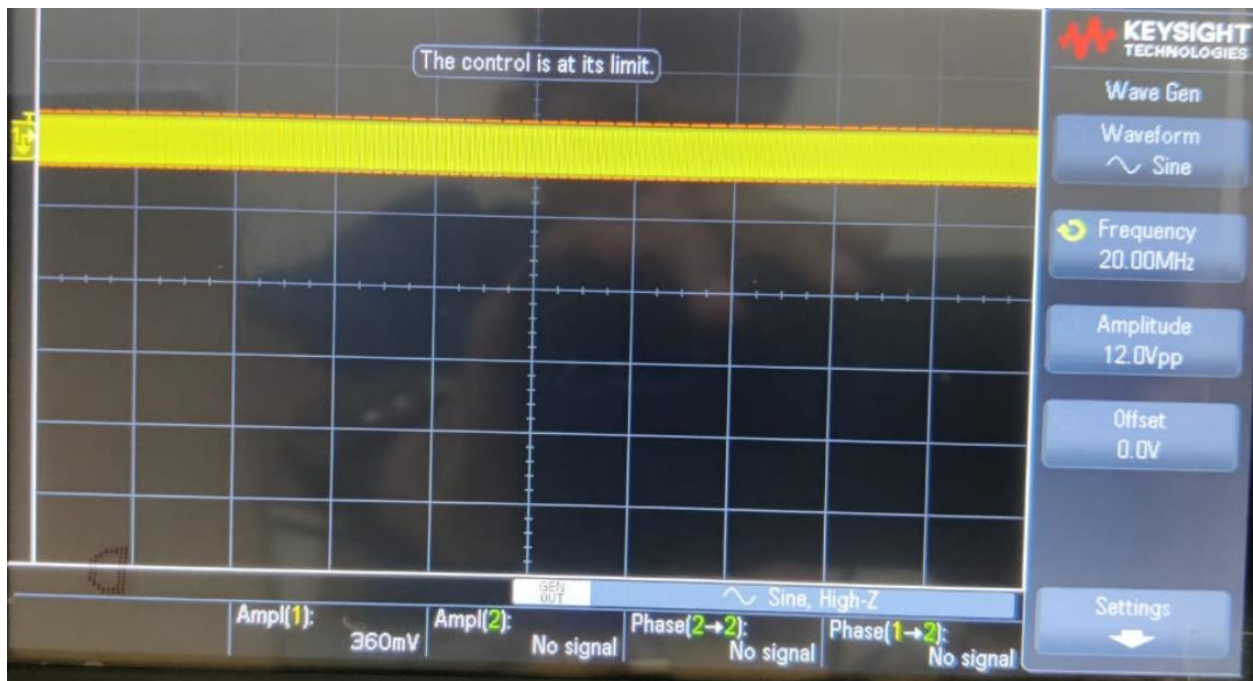

(d) Observation:→

At first the output amplitude increases till 1MHz and then significantly decreases.

Reason: On increasing the frequency, the bandwidth of the input cable is passed, After passing this frequency, there would be attenuation in the input signal.

frequency	Vp (Amplitude Vpeak-peak)
1 KHz	12.3V
10 KHz	12.1V
50 KHz	12.1V
100 KHz	12.3V
1 MHz	12.2V
5 MHz	12.2V
10 MHz	12.3V
20 MHz	12.2V

In my experiment
the Amplitude
of Vp doesn't gets decreased
∴ No reduction in input
side

Plots of Vp varying with frequency:


1-→1KHz




2->10KHz



3->50KHz:

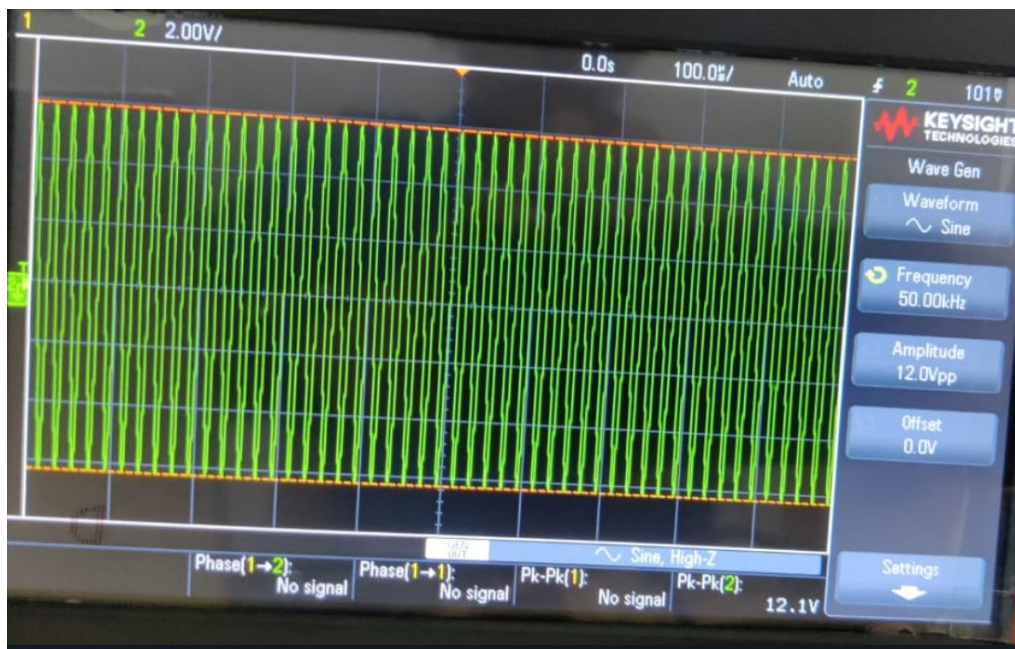


4->100KHz

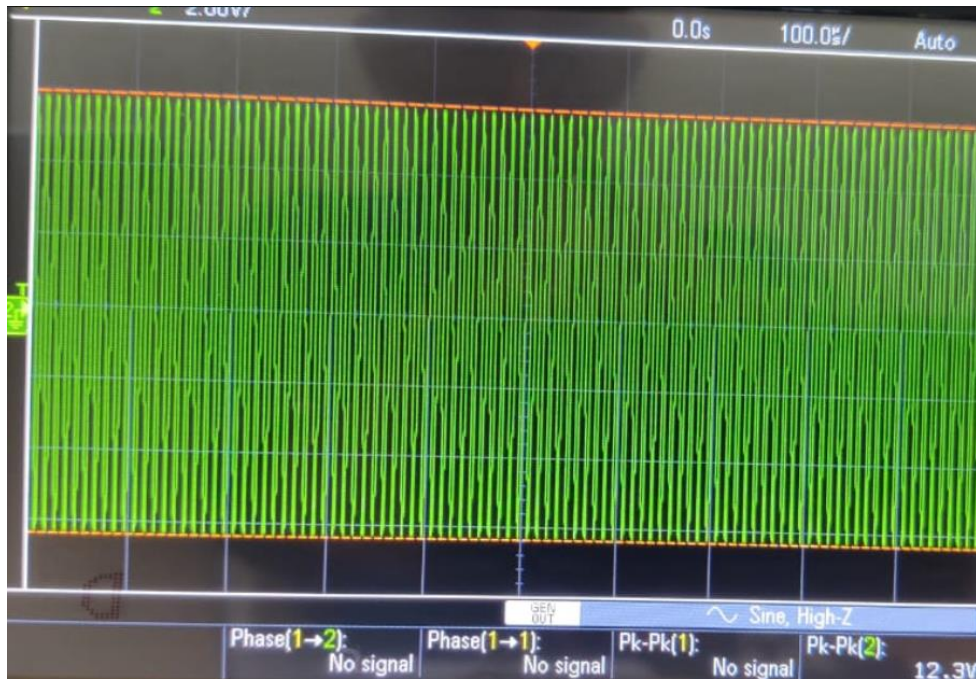


5->1MHz



6->5MHz

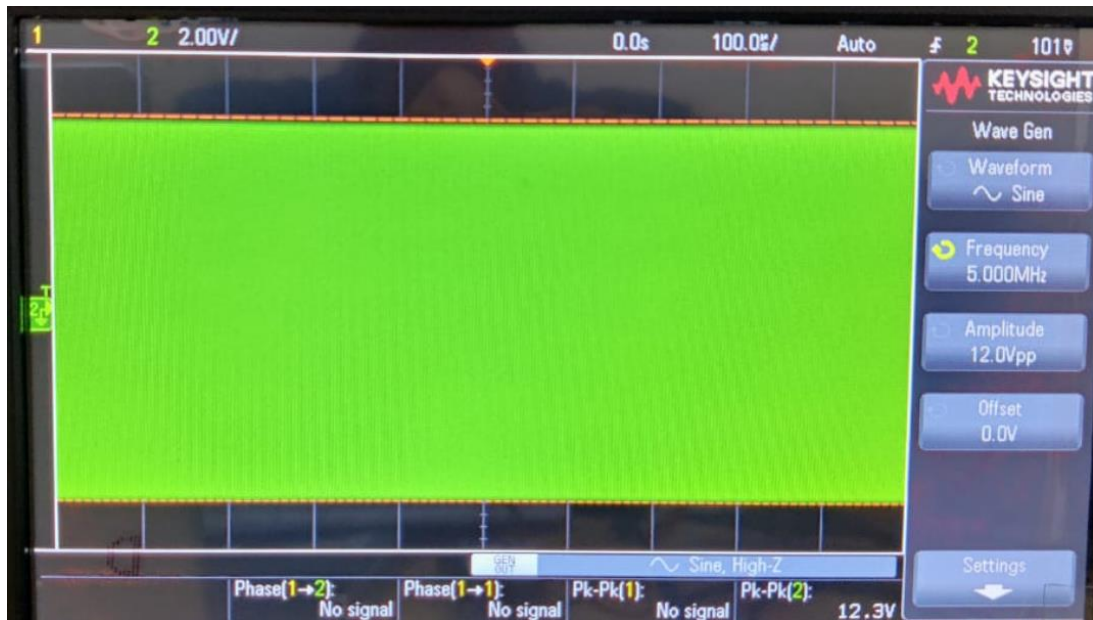

7->10MHz

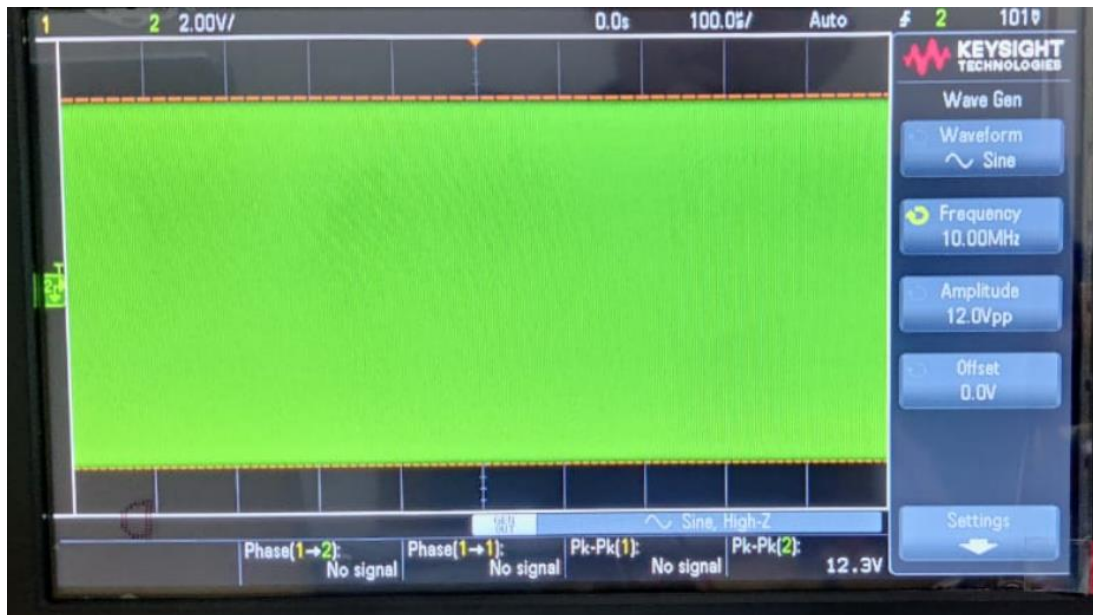


8- \rightarrow 20MHz




(c) As my V_{pp} is stable to 12.2V, there isn't any attenuation or decrease in frequency, therefore there doesn't exist a -3dB frequency for function generator output.

2. Full Wave Rectifier (FWR) using center tap transformer and two diodes


Schematic circuit:

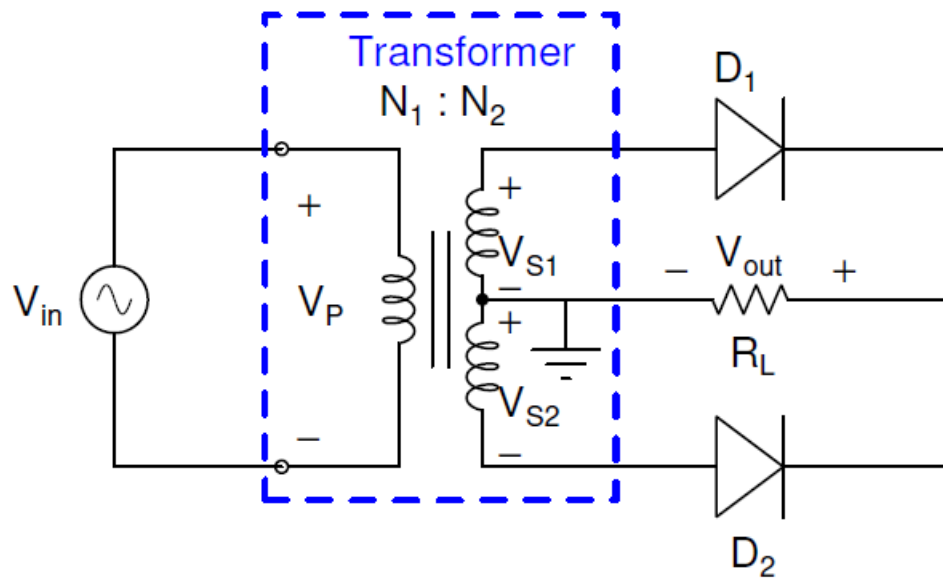


Circuit:

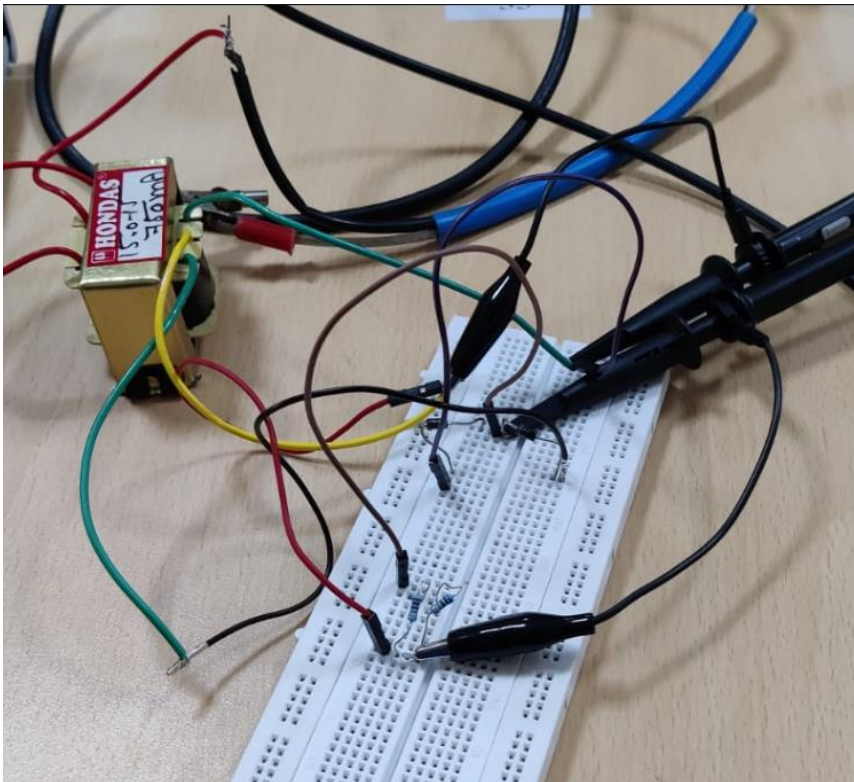

(b)

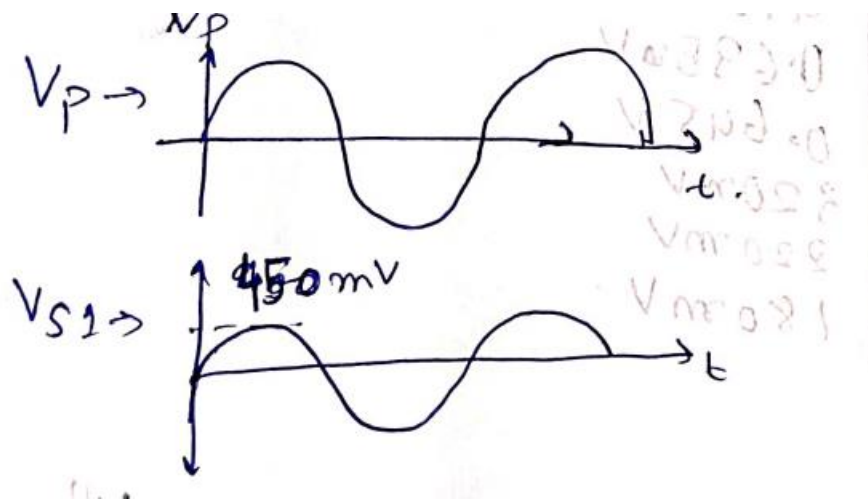

Vout:

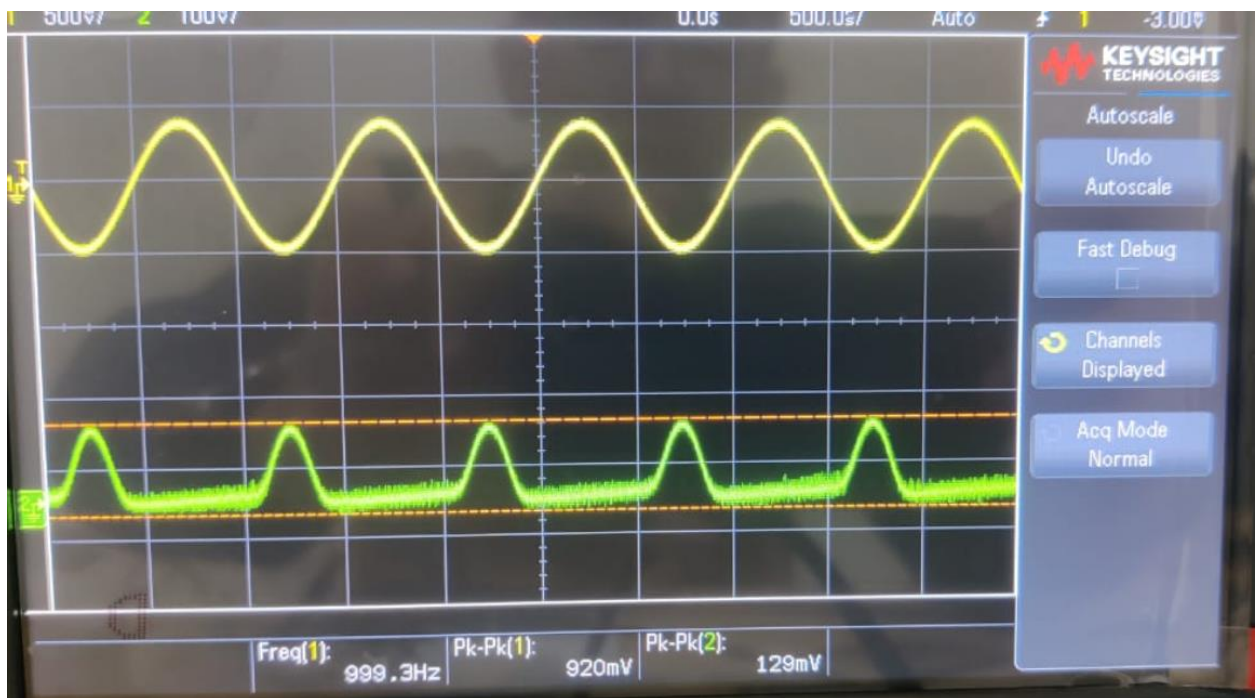

Amplitude: $V_{S1} = 460\text{ mV}$.

$V_{out} = 65\text{ mV}$.

My circuit is not giving full wave rectified output. The output is half wave rectified thought. I have checked all the connections, and also replace the diodes, but the graph is still half wave rectified.


(C) $I_{\text{peak}} = 65\text{mV}/50\text{ Kohm} = 1.29\text{ uA}$.

(d) Yes V_{out} amplitude is significantly reduced,
 The Reason is as the current is of μA range
 (0.5 uA) the diode is not completely in conduction
 mode, hence it doesn't allow much current
 so potential drop across R_L is very small.


3. Bridge rectifier for full wave rectification

Part A)


Circuit:

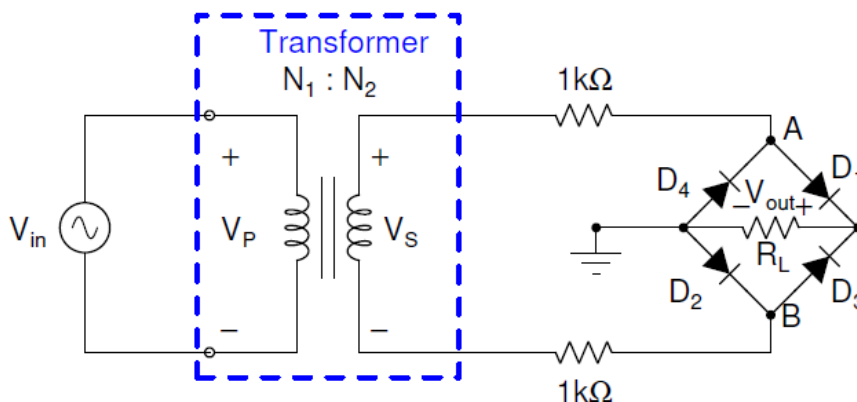

Circuit:

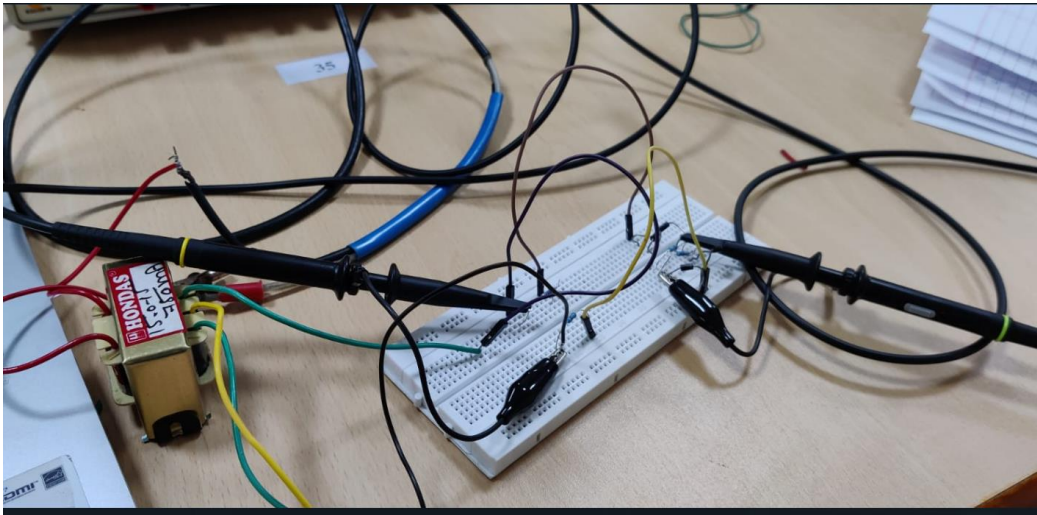

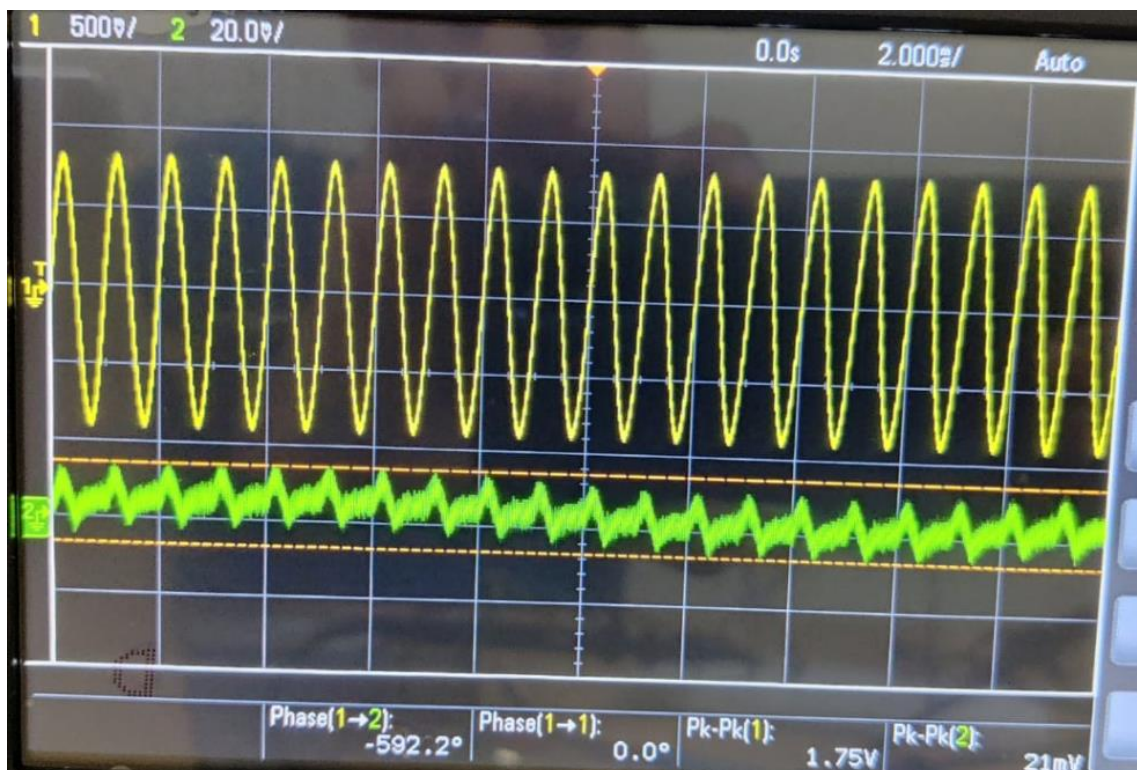Plotting V_s and V_{out} for the above circuit ($V_{pp(in)} = 12V$ and frequency: 50KHz):




$V_s \rightarrow V_{pp}$ value $\rightarrow 1.75\text{ v}$

$V_{out} \rightarrow V_{pp}$ value $\rightarrow 21mV$

$I_{peak} = 21mV / 50K\Omega = 0.42\mu A$


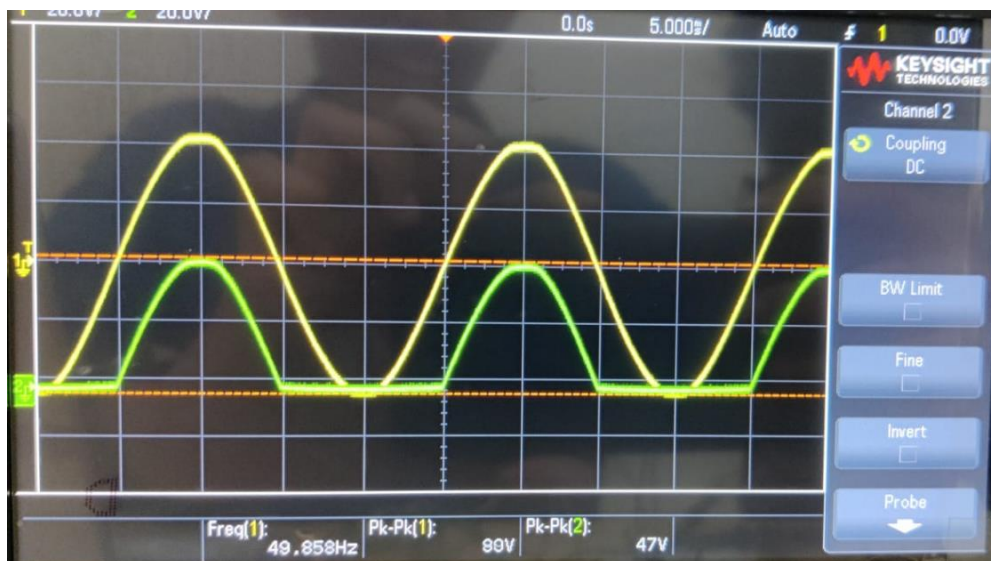
(d) Yes V_{out} amplitude is significantly reduced,
The Reason is as the current is of μA range
($0.5\mu A$) the diode is not completely in conduction
mode, hence it doesn't allow much current
so potential drop across R_L is very small. I_{in}

Plotting FWR output (V_{out}) for the wall supply:




Part B:

Schematic circuit:

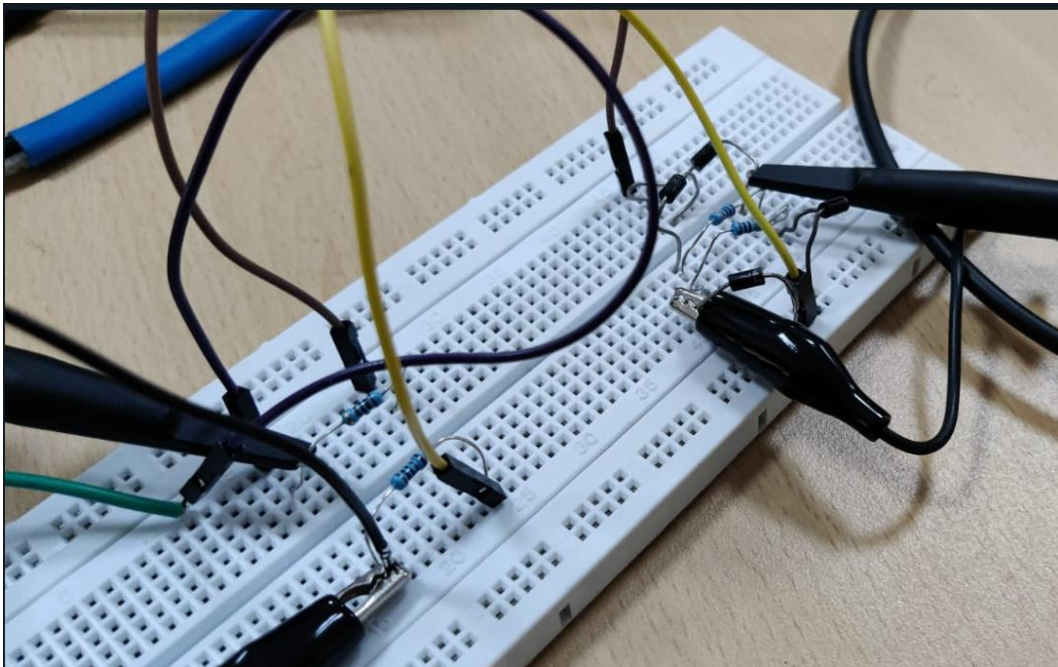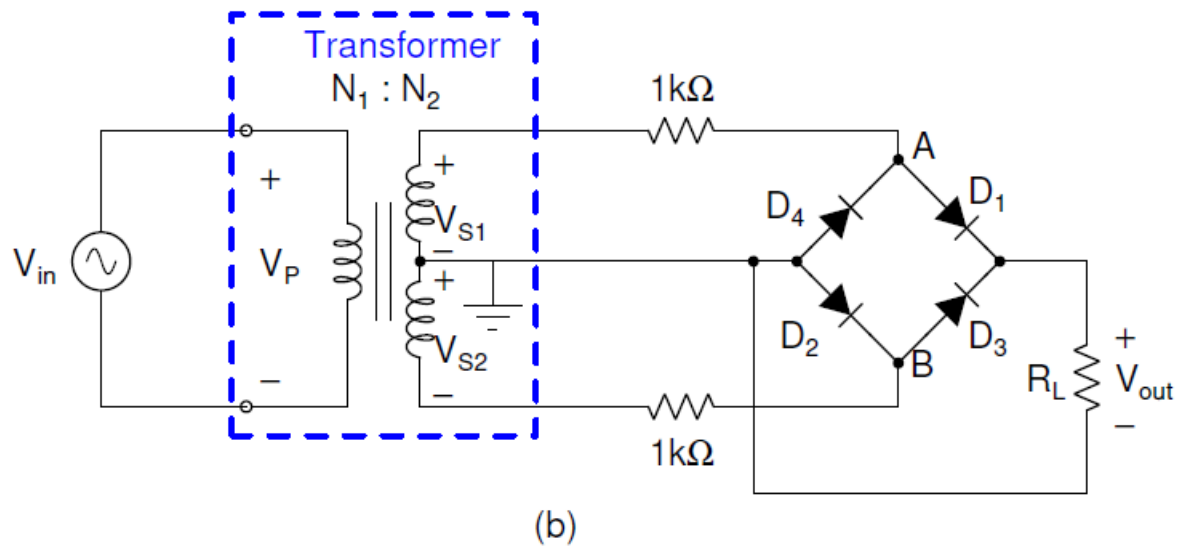

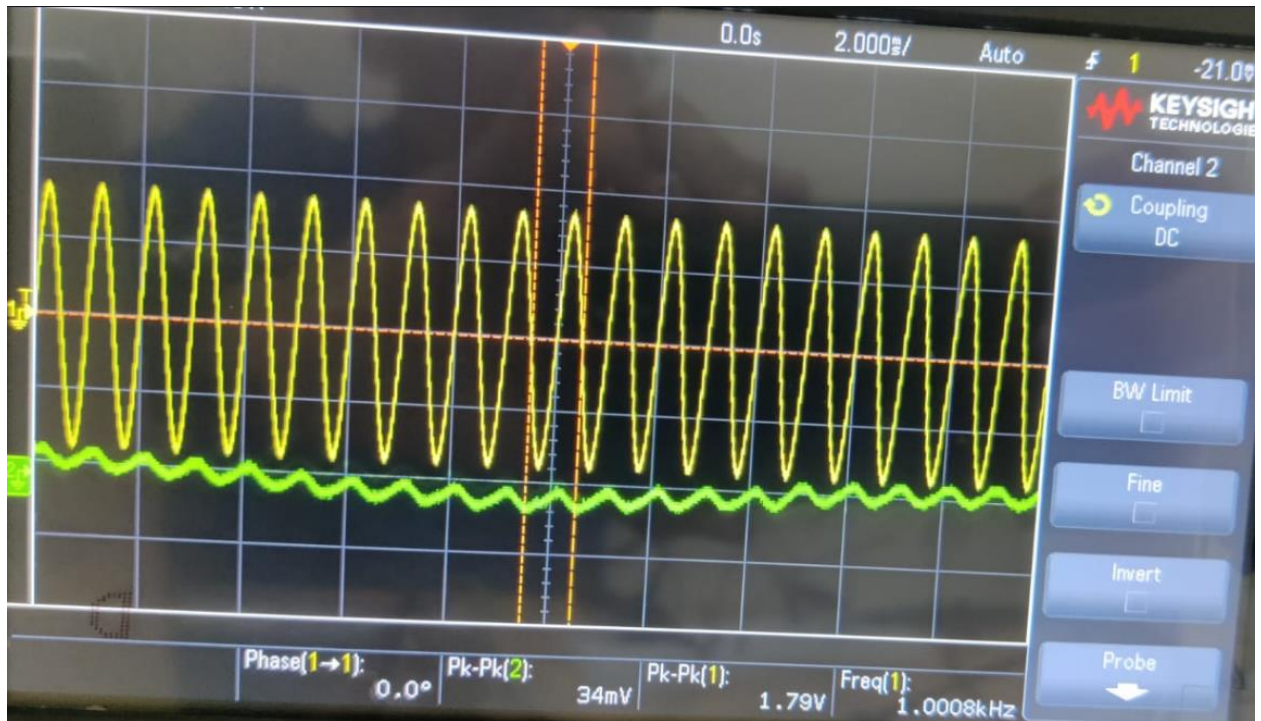Plotting V_s and V_{out} for the above circuit ($V_{ppin} = 12V$ and frequency: 50KHz):




$$(b) V_{S1} \rightarrow V_{PP} \rightarrow 450 \text{ mV}$$

$$V_{RL} = V_{PP} \rightarrow 17 \text{ mV}$$

$$\rightarrow (c) I_{\text{peak}} \Rightarrow \frac{17 \times 10^{-3}}{50 \times 10^3} \rightarrow \frac{17 \times 10^{-6}}{50} \rightarrow 0.34 \mu\text{A}$$

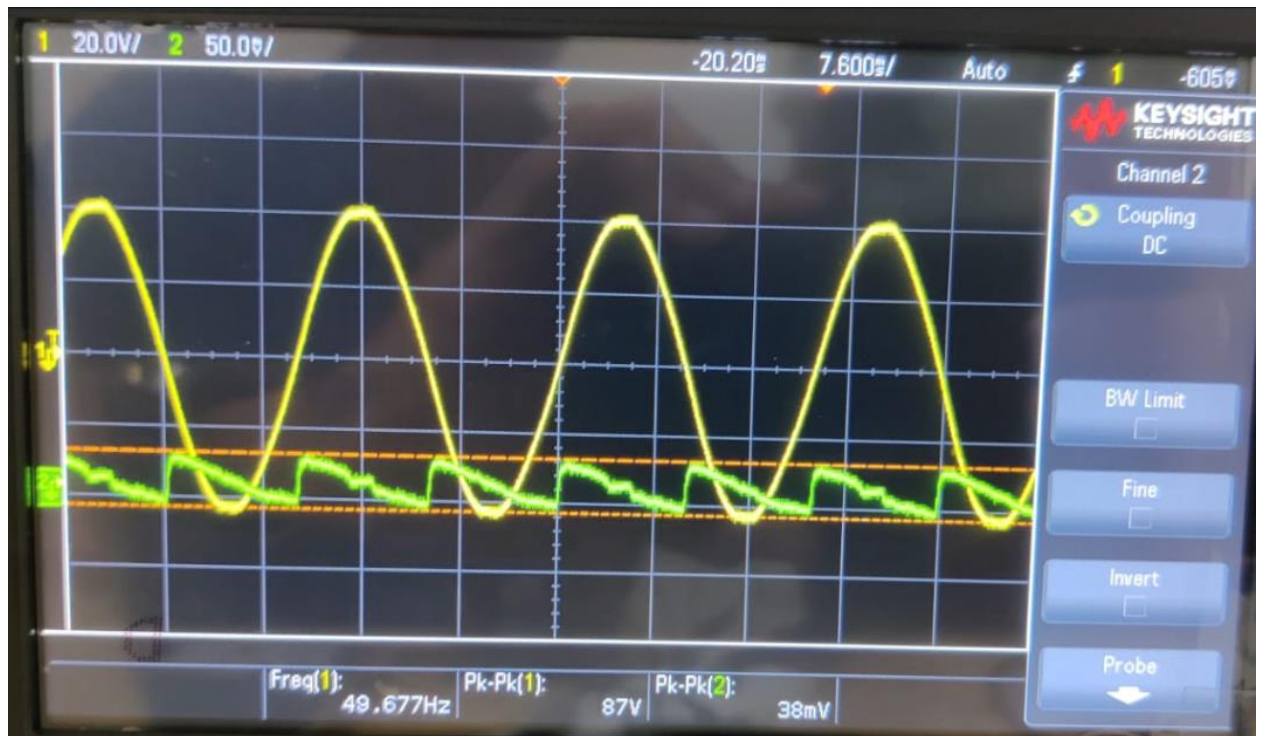Replacing V_{in} with the wall supply and plotting FWR output (V_{out}) for the wall supply:



We observe better signal levels at V_{out} as compared to the previous case when function generator was used as input source because the Voltage at secondary source is much higher than with Function generator, with function generator the peak-to-peak value was 900mv whereas here it is 87V, that is much higher and so the diodes conduct fully in forward bias condition. Hence, we get a clearer graph.