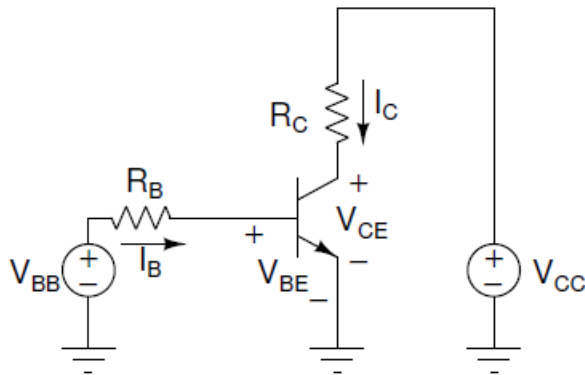


Experiment-4


BJT characterization

1. BJT Characterization

Schematic view of Circuit:



Circuit:

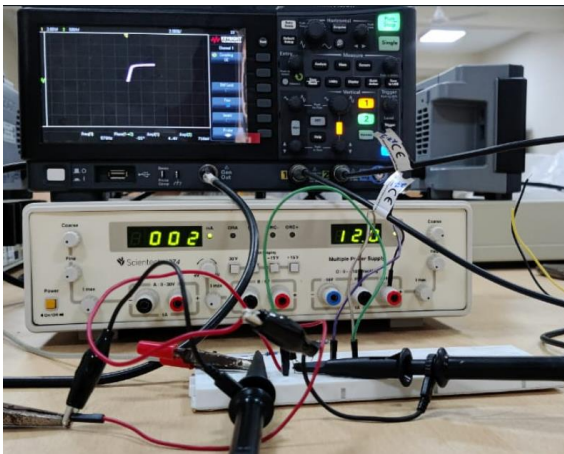


Plotting V_{BE} (CH2) (Y-axis) vs V_{BB} (CH1) (X-axis) for $V_{BB} = 0 \text{ V}$ to $V_{BB} = 4 \text{ V}$.

$V_{BB} = \{0.2, 0.3, 0.4, 0.5, 0.6, 0.7, 0.8, 0.9, 1, 1.2, 1.4, 1.6, 1.8, 2, 3 \text{ and } 4\} \text{ V}$.

Also plotting V_{BB} (X-axis) vs V_{CE} (Y-axis)

Plots(V_{BE} (CH2) (Y-axis) vs V_{BB} (CH1) (X-axis)):

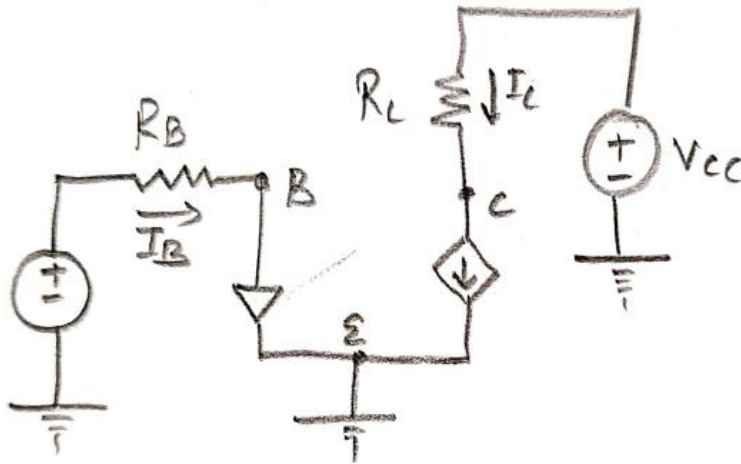The large signal model of the above circuit:



For V_{BE} (CH2) (Y-axis) vs V_{BB} (CH1) (X-axis) plot initially when we increase V_{BB} from 0 to cut in voltage of the model diode, the diode hasn't reached its cut-in voltage and passes very low current hence there is no loss across R_B because the current is very small, therefore V_B will nearly be equal to V_{BB} .


After V_{BB} reaches cut in voltage the voltage across diode which is equal to V_{BE} is nearly constant to cut in voltage.

Hence such plot is achieved.

$$1. V_{BB} = 0.3V$$



$$2. V_{BB} = 0.6V$$

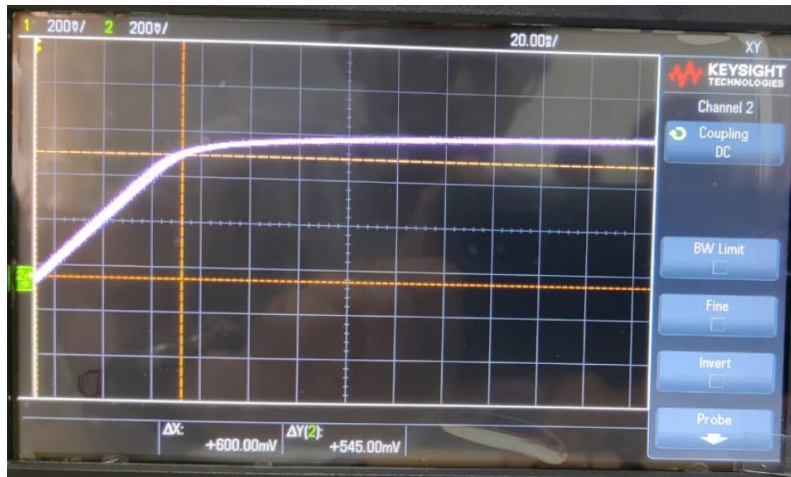

$$3. V_{BB} = 1V$$



4. $V_{BB} = 1.4V$




5. $V_{BB} = 2V$




6. $V_{BB} = 3V$



6. $V_{BB} = 4V$

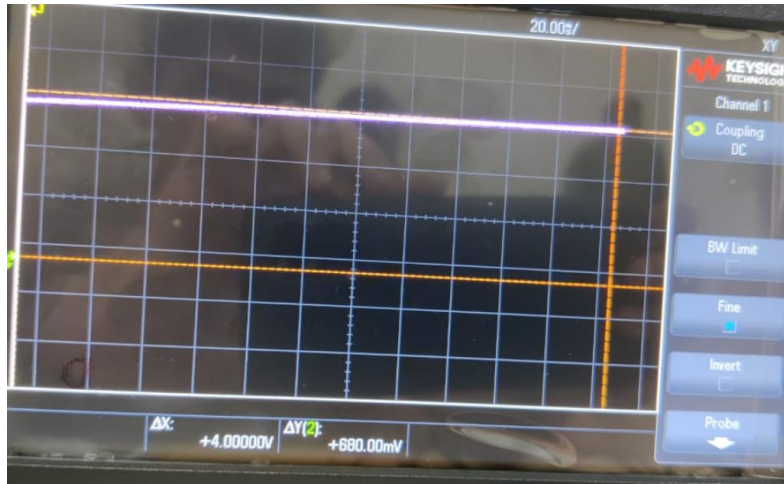


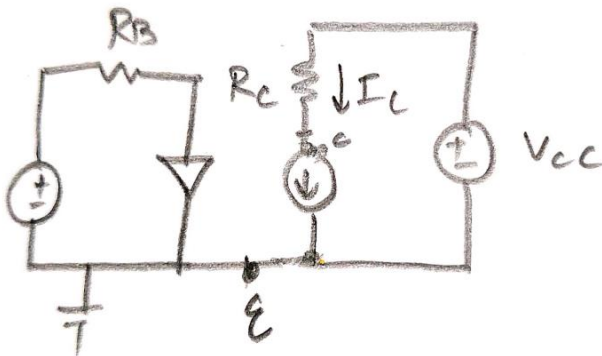Plotting V_{BB} (X-axis) vs V_{CE} (Y-axis):




Explaining the plot of V_{BB} (X-axis) vs V_{CE} (Y-axis). In the large signal model as seen above when V_{BB} is low, V_{BE} is equal to V_{BB} which are very low, as a result the V_{BE} is also low, because of which I_C is also not significant, not producing much loss across the R_C resistance, therefore the collector emitter voltage will be V_{CC} . At higher values of V_{BB} the V_{BE} value also increases(after sometime nearly constant), because increasing V_{BE} the I_C current value also increases, producing greater potential loss across the R_C , hence decreasing the value of V_C .


1. $V_{BB} = 0.2V$

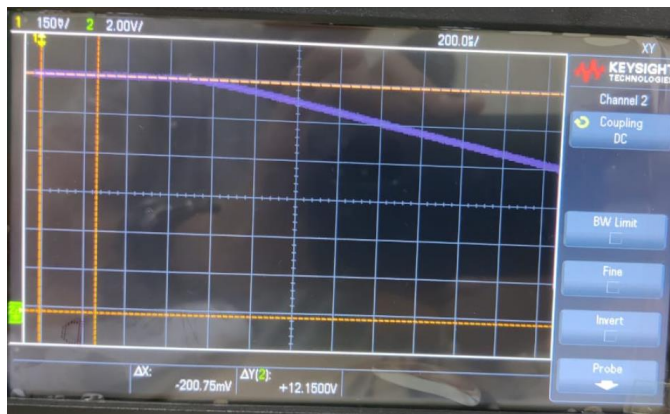


2. $V_{BB} = 0.6V$

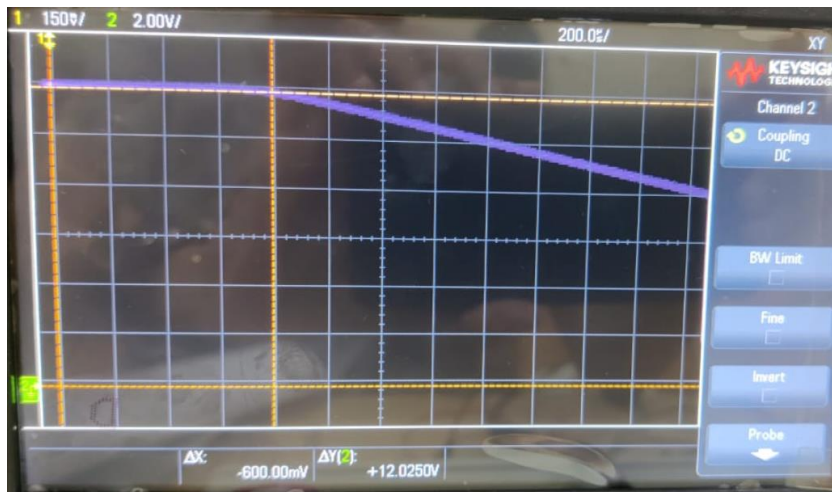

3. $V_{BB} = 0.9V$

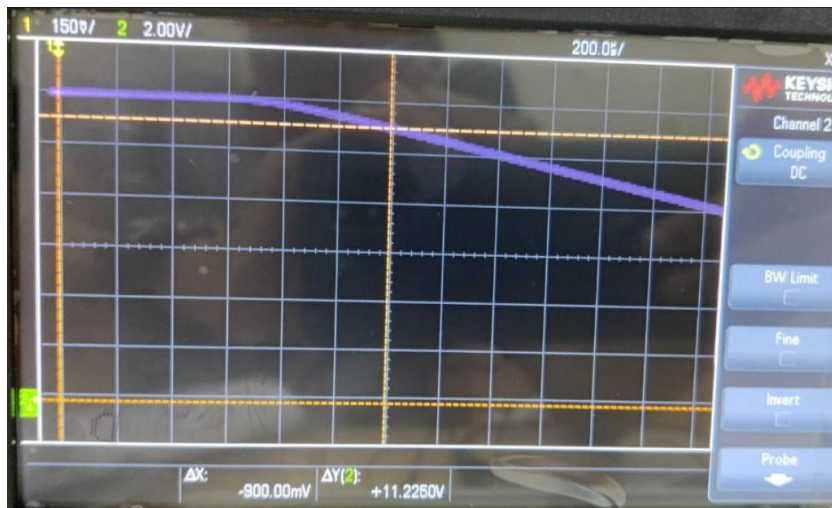


4. $V_{BB} = 1.2V$

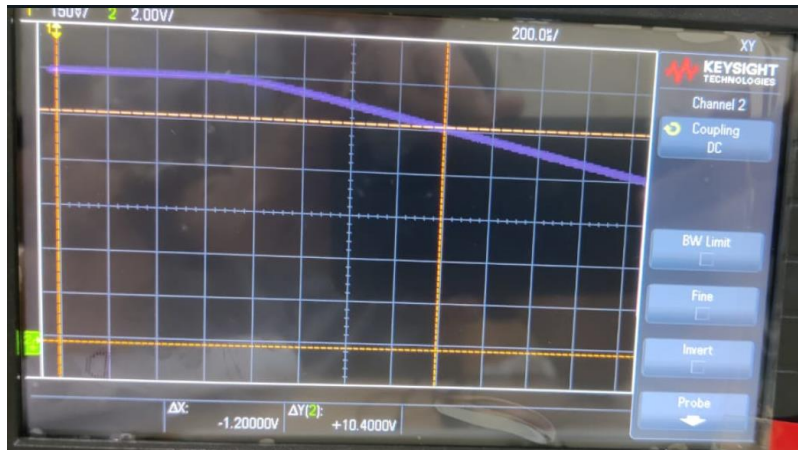


5. $V_{BB} = 1.6V$



6. $V_{BB} = 2V$

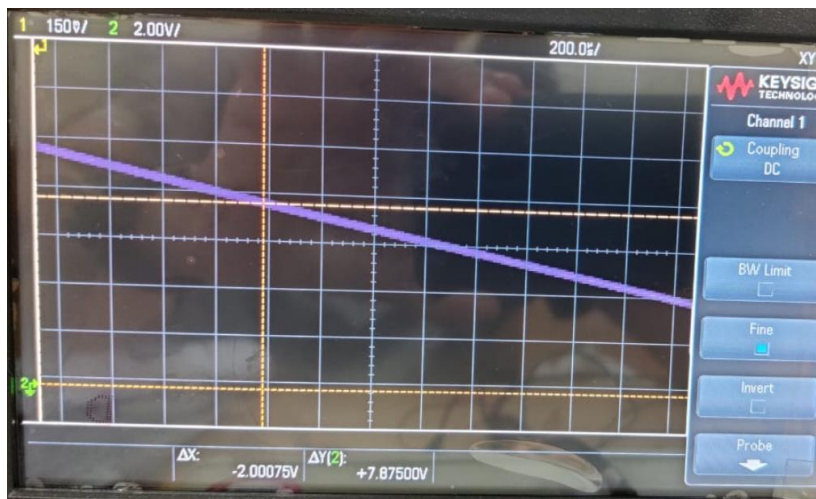

7. $V_{BB} = 3V$

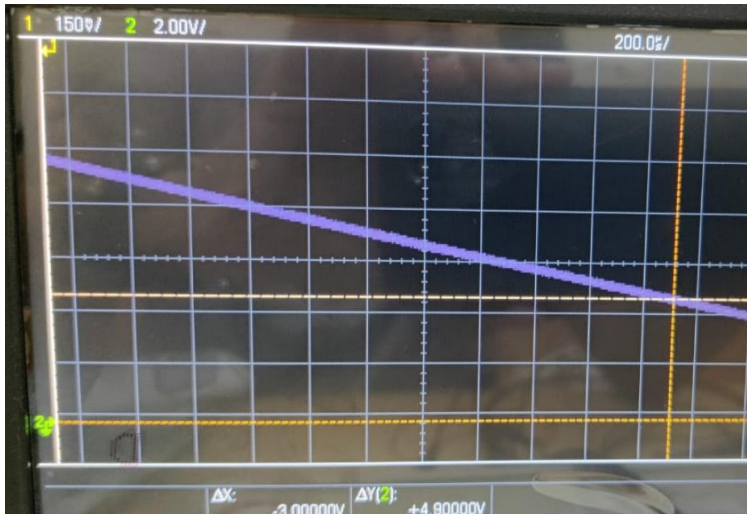

8. $V_{BB} = 4V$



Tabulating the found values and finding currents and β .

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}, I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

$V_{CC} = 12.3 V$

V_{BB} (V)	V_{BE} (mV)	I_B (A)	V_{CE} (V)	I_C	β	Mode
0.2	190	1e-006	12.15	0.00015	150	Active
0.3	290	1e-006	12.15	0.00015	150	Active
0.4	380	2e-006	12.15	0.00015	150	Active
0.5	482	1.8e-006	12.15	0.00015	150	Active
0.6	545	5.5e-006	12.025	0.00019	34.544	Active

0.7	582	1.18e-005	11.8	0.0002	16.9492	Active
0.8	595	2.05e-005	11.525	0.000475	23.1707	Active
0.9	602	2.98e-005	11.225	0.000775	26.0067	Active
1	610	3.9e-005	10.925	0.001075	27.5641	Active
1.2	627.5	5.72e-005	10.400	0.0016	27.972	Active
1.4	640	7.6e-005	9.725	0.002275	29.9342	Active
1.6	642.5	9.57e-005	9.100	0.0029	30.303	Active
1.8	647.5	0.00011525	8.450	0.00355	30.8026	Active
2	647.5	0.00013525	7.875	0.004125	30.4991	Active
3	667.5	0.00023325	4.900	0.0071	30.4394	Active
4	680	0.000332	2.0750	0.009925	29.8946	Saturation

2. BJT Output Characteristics (I_c vs V_{ce})

Schematic view of the circuit:



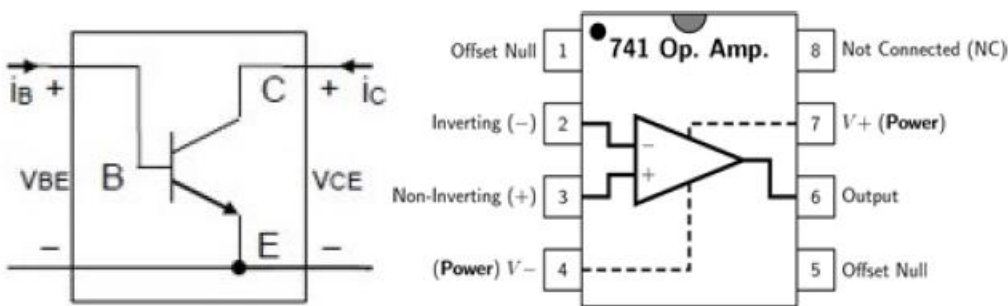
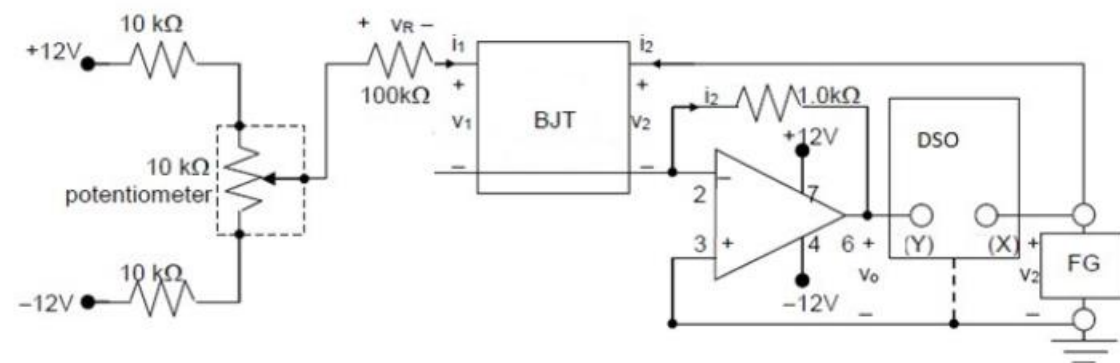



Figure 3: (a) NPN BJT, (b) opamp pin configuration

Circuit:

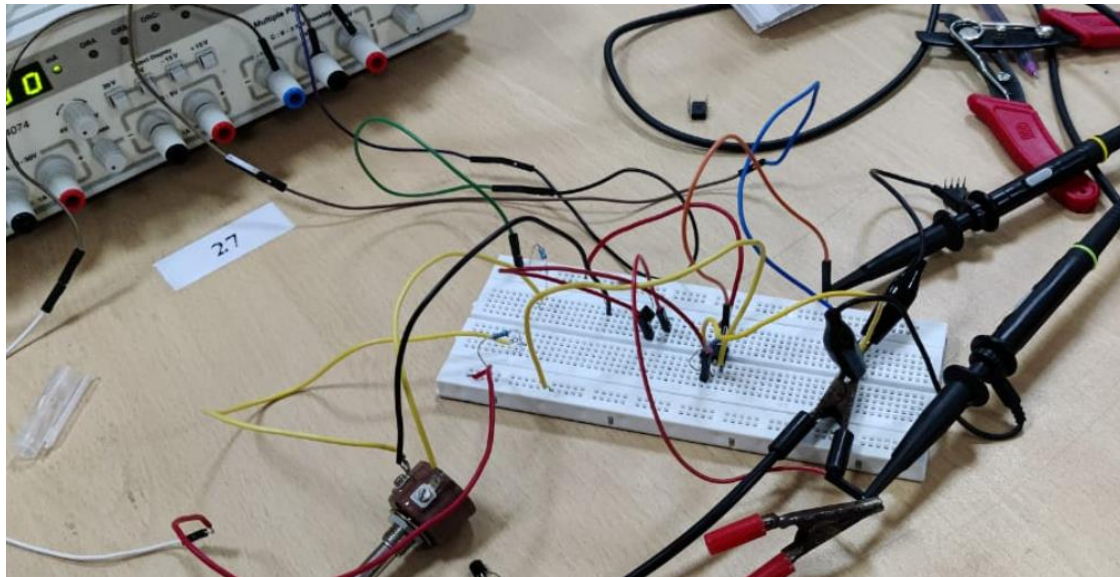

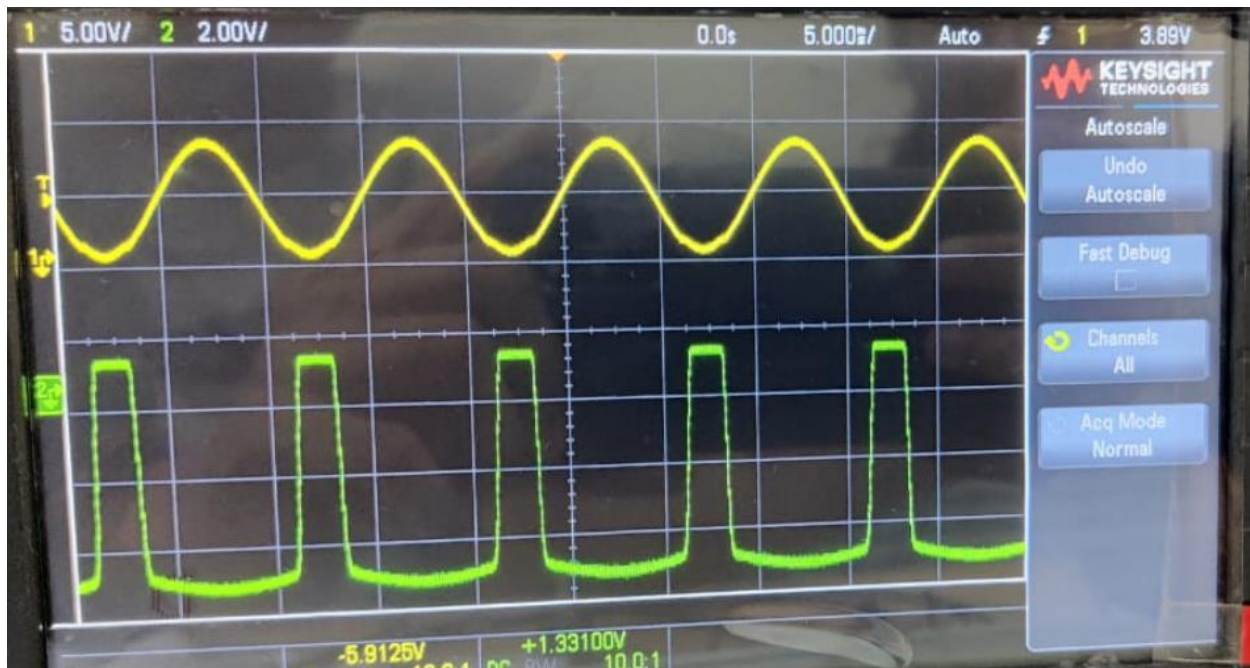
Plots on the OSC of $V_2(V_{CE})$ and V_O :



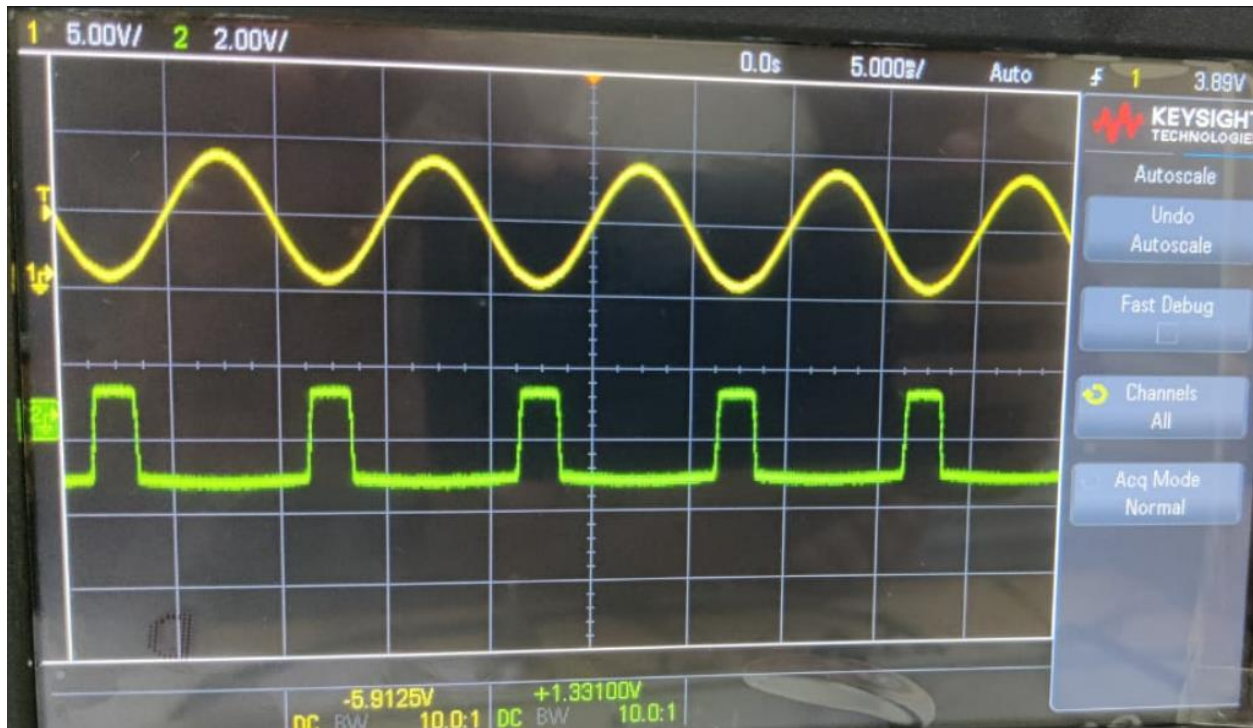

$V_2 = V_{CE}$ and $V_0 (\propto -I_c)$ are found using OSC, we are plotting V_{CE} vs V_0 x-y characteristic on OSC and measuring its value at different V_{BB} values. As we cannot measure all the V_{CE} and V_{BB} , we are measuring only two values, one in saturation and one in active region.

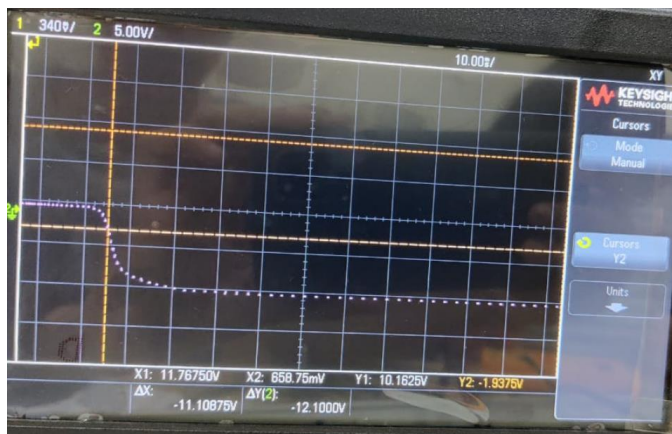We will see different values of V_{CE} and V_{be} , by varying V_{bb} using potentiometer, we will also be measuring the values of V_{be} using a multimeter.



The x-y characteristic plot comes as shown above, before cut in voltage, i.e in saturation region the $V_0 (\propto -I_C)$ increases as V_{CE} increase, but after crossing the cut in voltage the value of $V_0 (\propto -I_C)$ is constant because collector current does not depend on V_{CE} , it only depends on V_{BE} . On increasing the value of V_{BB} , the magnitude of active region $V_0 (\propto -I_C)$ because I_C increases with increase in V_{BE} , and increase in V_{BB} increases V_{BE} .

Plots and multimeter readings:


We will be measuring value of V_0 at $V_{CE} = 658.75\text{mV}$ (saturation region) and $V_{CE} = 4\text{V}$ (Active region).

1. $V_{BB} = 4\text{V}$

V_{BE} :



V_0 (saturation region):

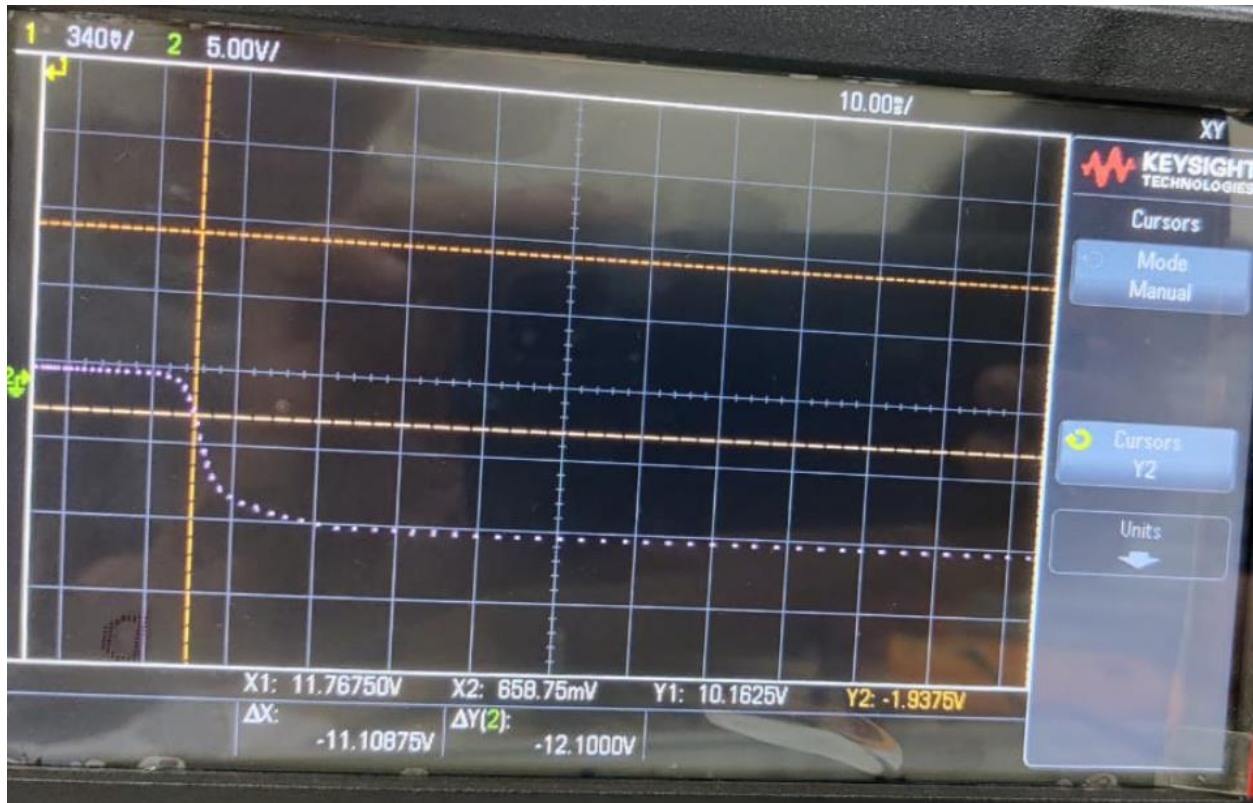

V_o (Active region):


I forgot to take an image in this region for $V_{BB} = 4V$.

2. $V_{BB} = 2V$


V_{BE} :



V_o (saturation region):

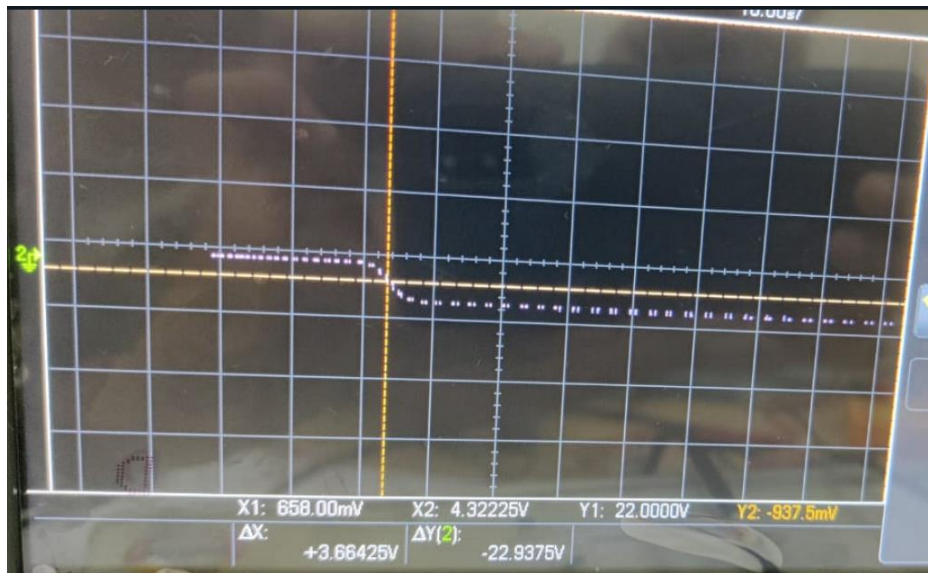


V_o (Active region):

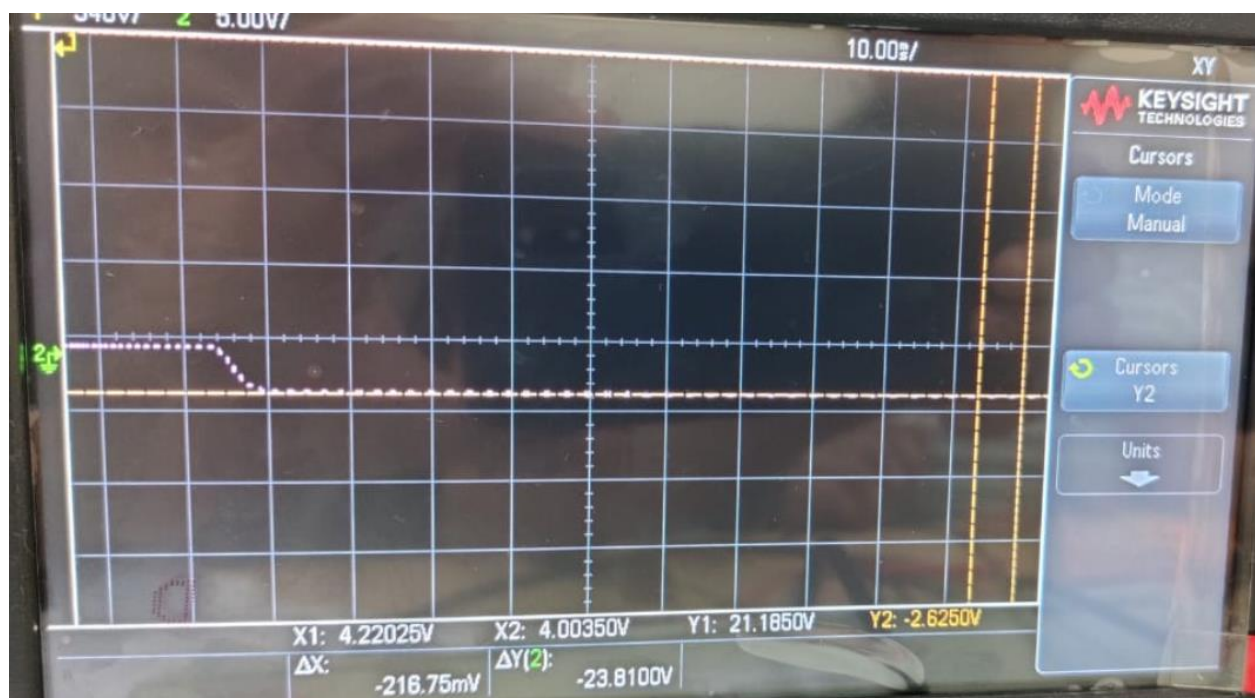


3. $V_{bb} = 1V$



V_o (saturation region):

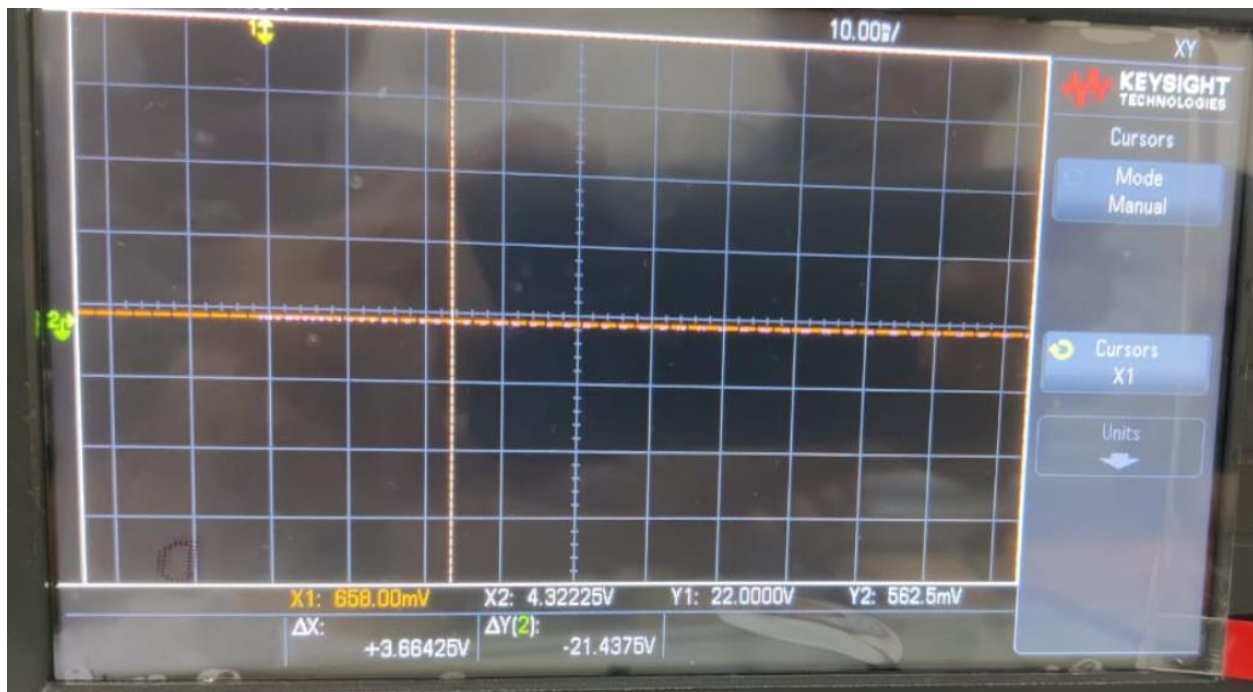

V_o (Active region):

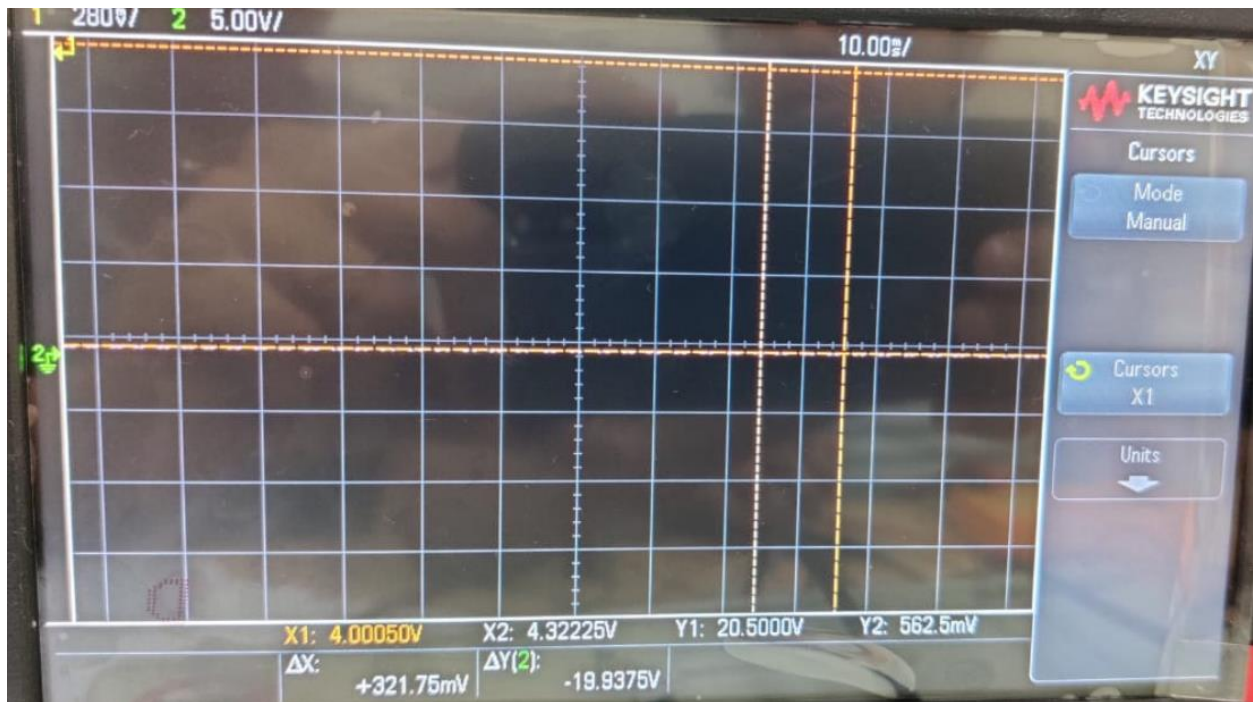


1. $V_{bb} = 0.5V$



V_o (saturation region):



Vo(Active region):

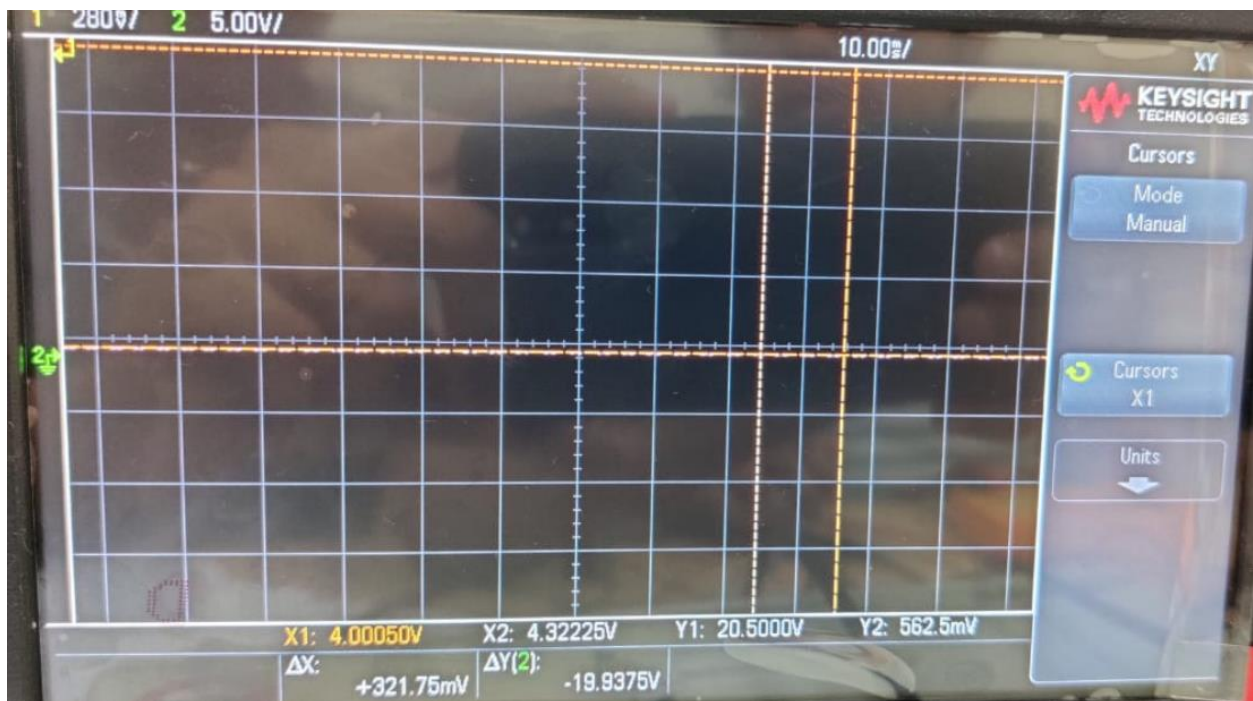


1. $V_{bb} = 0.2V$



V_o (saturation region):



V_o (Active region):

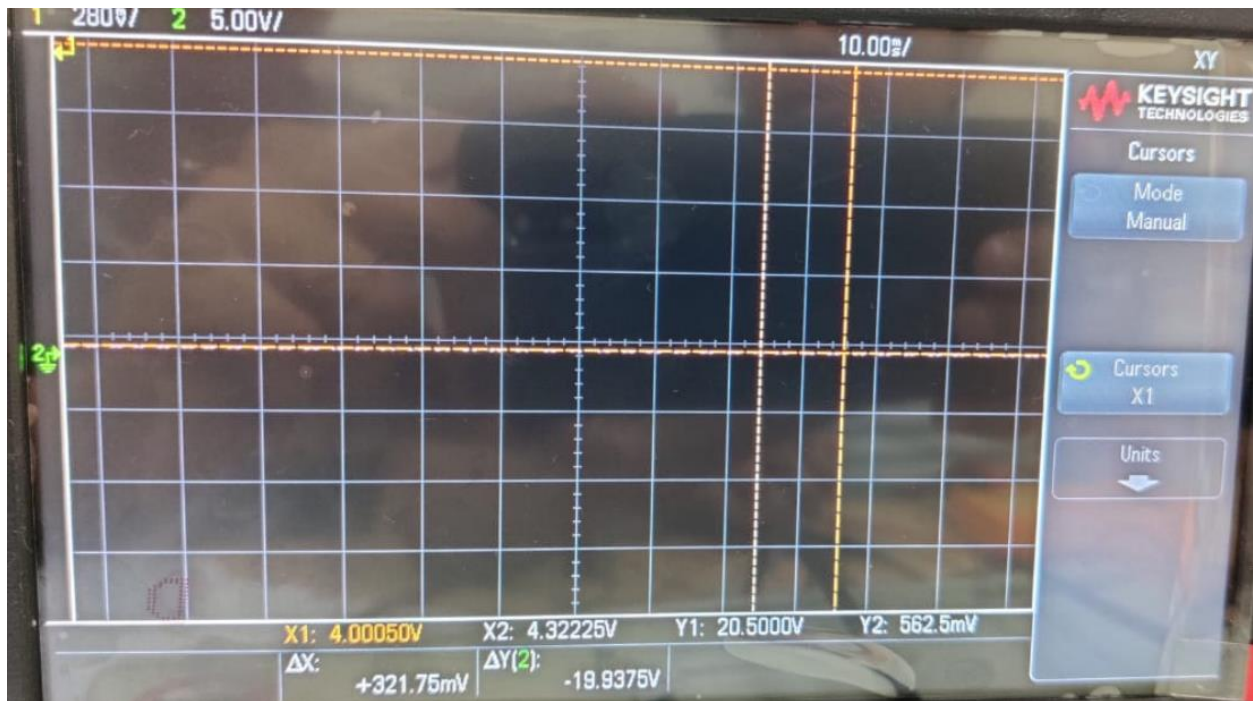

$$V_{BB} - I_B R = V_{BE}$$

$$I_B = (V_{BB} - V_{BE}) / R$$

$$R = 100K \Omega.$$

V_B	V_{BE}	I_B (A)	V_{CE} Saturation mode	V_o Saturation mode	I_C Saturation mode	V_{CE} Active mode	V_o Active mode
4V	0.60V	3.4e-005	658.75mV	-1.9375V	1.9375mA	4V	-9.25V
2V	0.56V	1.44e-005	658.75mV	-937.5mV	937.5uA	4V	-2.6250V
1V	0.25V	7.5e-006	658.75mV	-562.5mV	562.5uA	4V	-582.5mV
0.5V	0.06V	4.4e-006	658.75mV	-562.5mV	562.5uA	4V	-582.5mV
0.2V	-0.11V	3.1e-006	658.75mV	-562.5mV	562.5uA	4V	-582.5mV

B (I_C/I_B) (Saturation region).
5.698
65.104
75
127.841
181.452